

VTU VHDL LAB MANUAL



1617, "SLN", 14th Cross, 1st Stage, 2nd Phase, Chandra Layout,
Bangalore-560072.
Telefax : 080 - 23217306
info@rampplus.com
www.rampplus.com

Experiment 1: Write VHDL code for realize all logic gates.

- a) **AND Gate:** A Logic circuit whose output is logic ‘1’ if and only if all of its inputs are logic ‘1’.


Truth table

Inputs		Output
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$Y = A \text{ AND } B$$

$$= A.B$$

Logic diagram

 

VHDL Code for AND Gate:



```

-----
-- File           :    andgate.vhd
-- Entity         :    andgate
-----
-- University     :    Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     :    Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   :    Xilinx ISE
-- Target Device  :    Spartan II or XC Series
-----
-- Description    :    VHDL code to realize AND gate functionality
-----
--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----
entity andgate is
    Port( A : in  std_logic;
          B : in  std_logic;
          Y : out std_logic
        );
end andgate;

architecture Behavioral of andgate is
begin
    Y<= A and B ;
end Behavioral;

```

VHDL LAB MANUAL

 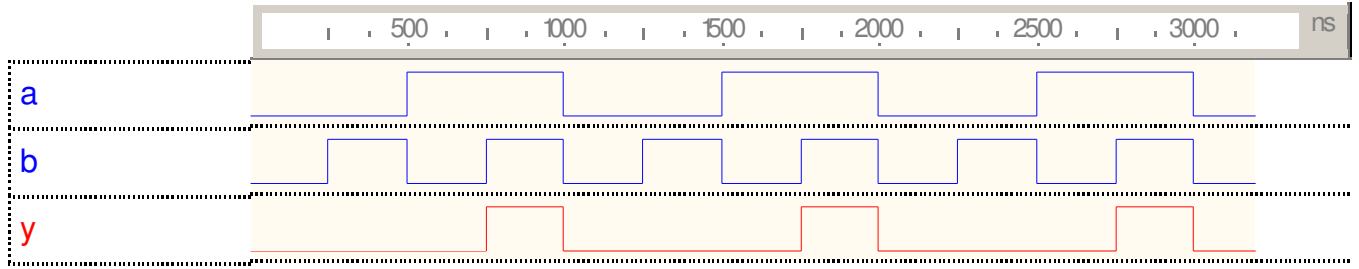

RTL VIEW

b)OR Gate: A logic gate whose output is logic '0' if and only if all of its inputs are logic '0'.


Truth table

Inputs		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

$$Y = A \text{ OR } B$$

$$= A + B$$

Logic diagram

 

VHDL Code for OR Gate:

```


-----
-- File           : orgate.vhd
-- Entity         : orgate
-----
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     : Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   : Xilinx ISE
-- Target Device  : Spartan II or XC Series
-----
-- Description    : VHDL code to realize OR gate functionality
-----

```

VHDL LAB MANUAL

```
--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----
entity orgate is
    Port( A : in  std_logic;
          B : in  std_logic;
          Y : out std_logic
        );
end orgate;

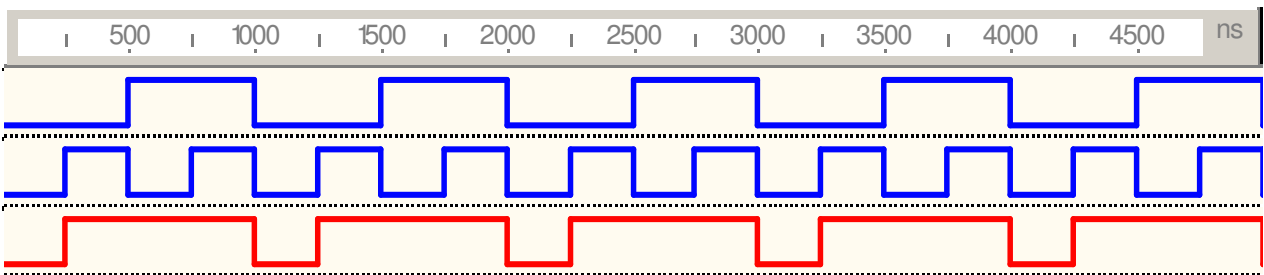architecture Behavioral of orgate is
begin
    Y<= A or B ;
end Behavioral;
```




c) NOT Gate: A logic gate whose output is complement of its input.

Truth table

Input	Output
A	Y
0	1
1	0

Logic diagram

 

$$Y = \text{NOT } A$$

VHDL Code for NOT Gate:

```
-----
-- File           : notgate.vhd
-- Entity         : notgate
-----
```

```
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     : Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   : Xilinx ISE
-- Target Device  : Spartan II or XC Series
```

VHDL LAB MANUAL

```
-----
-- Description      :      VHDL code to realize NOT gate functionality
-----
```

```
--The IEEE standard 1164 package, declares std_logic, etc.
```


```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
```

```
----- Entity Declarations -----
```

```
entity notgate is
    Port( A : in  std_logic;
          Y : out std_logic
        );
end notgate;
```

```
architecture Behavioral of notgate is
```
 
```
begin
    Y<= not A ;
end Behavioral;
```




d) NAND Gate: A logic gate which gives logic '0' output if and only if all of its inputs are logic '1'

Truth table

Inputs		Output
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Logic diagram

 

$$Y = A \text{ NAND } B$$

$$= (A \cdot B)'$$

VHDL Code for NAND Gate:

```
-----
-- File           :      nandgate.vhd
-- Entity         :      nandgate
-----
```

VHDL LAB MANUAL

```
-- University      : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     : Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   : Xilinx ISE
-- Target Device  : Spartan II or XC Series
```

```
-- Description    : VHDL code to realize NAND gate functionality
```

```
--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
```

```
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
```

```
----- Entity Declarations -----
```

```
entity nandgate is
    Port( A : in  std_logic;
          B : in  std_logic;
          Y : out std_logic
        );
```


```
end nandgate;
```

```
architecture Behavioral of nandgate is
```

```
begin
```

```
    Y<= A nand B ;
```

```
end Behavioral;
```

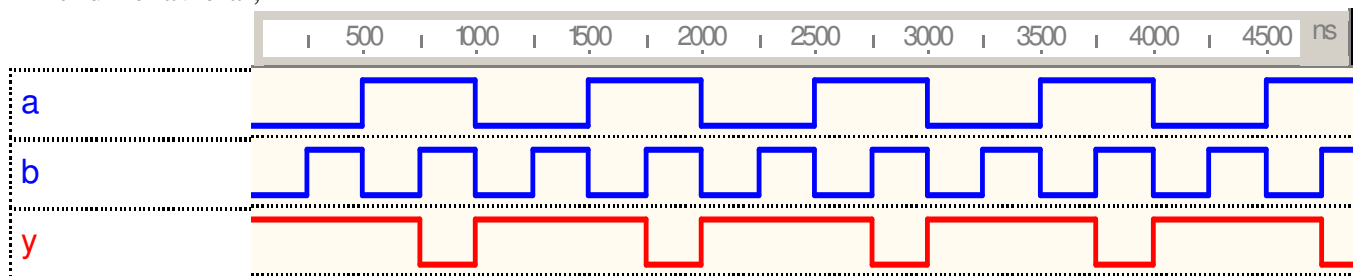


e) **NOR Gate:** A logic gate whose output logic '1' if and only if all of its inputs are logic '0'

Truth table

Inputs		Output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Logic diagram

 

$$Y = A \text{ NOR } B$$

$$= (A + B)'$$

VHDL Code for NOR Gate:

VHDL LAB MANUAL

```
-- File           : norgate.vhd
-- Entity        : norgate
-----
-- University    : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators    : Mentor Graphics Modelsim OR Active HDL
-- Synthesizers  : Xilinx ISE
-- Target Device : Spartan II or XC Series
-----
-- Description   : VHDL code to realize NOR gate functionality
-----
```

--The IEEE standard 1164 package, declares std_logic, etc.

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
```


----- Entity Declarations -----

```
entity norgate is
    Port( A : in std_logic;
          B : in std_logic;
          Y : out std_logic
        );
```

```
end norgate;
```

```
architecture Behavioral of norgate is
begin
```
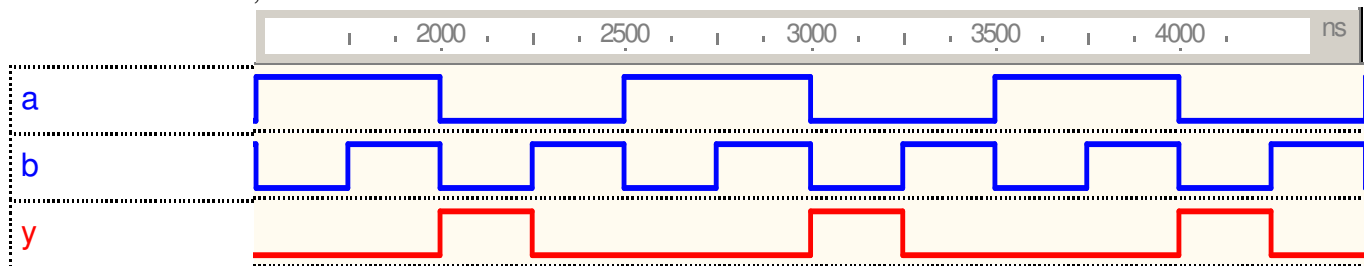
```
    Y<= A nor B ;
end Behavioral;
```




f) **EX-OR (Exclusive OR):** A logic gate whose output is logic '0' when all the inputs are equal and logic '1' when they are unequal.

Truth table

Inputs		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Y= A EX-OR B
= A (+)B

Logic diagram

 


VHDL LAB MANUAL

$$= A.B\ + A\ .B$$

VHDL Code for EX-OR Gate:

```
-----  
-- File           :    xorgate.vhd  
-- Entity         :    xorgate  
-----  
-- University     :    Directorate of Technical Education, VLSI Design Lab V E&C  
-- Simulators     :    Mentor Graphics Modelsim OR Active HDL  
-- Synthesizers   :    Xilinx ISE  
-- Target Device  :    Spartan II or XC Series  
-----  
-- Description    :    VHDL code to realize EX-OR gate functionality  
-----  
--The IEEE standard 1164 package, declares std_logic, etc.  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
----- Entity Declarations -----  
entity xorgate is  
    Port( A : in  std_logic;  
          B : in  std_logic;  
          Y : out std_logic  
        );  
end xorgate;  
  
architecture Behavioral of xorgate is  
begin  
    Y<= A xor B ;  
end Behavior ;
```

 


g) EX-NOR (Exclusive -NOR) gate: A logic gate that produces a logic '1' only when the two inputs are equal

Truth table

Logic diagram

VHDL LAB MANUAL

Inputs		Output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

 

$$\begin{aligned}
 Y &= A \text{ XNOR } B \\
 &= (A (+)B) \setminus \\
 &= (A.B) \setminus + A.B
 \end{aligned}$$

VHDL Code for EX-NOR Gate:

```

-----
-- File           :    xnorgate.vhd
-- Entity         :    xnorgate
-----
-- University     :    Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     :    Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   :    Xilinx ISE
-- Target Device  :    Spartan II or XC Series
-----
-- Description    :    VHDL code to realize EX-NOR gate functionality
-----

```

```

--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;

```

```

use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----

```

```

entity xnorgate is
    Port( A : in  std_logic;
          B : in  std_logic;
          Y : out std_logic
        );

```

```


end xnorgate;
architecture Behavioral of xnorgate is
begin

```

```



    Y<= A xnor B ;
end Behavioral;

```

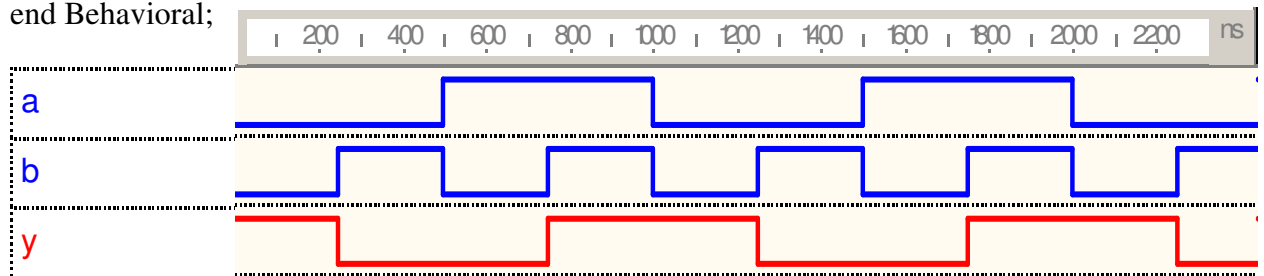

Experiment 2: Write a VHDL program for the following combinational designs.

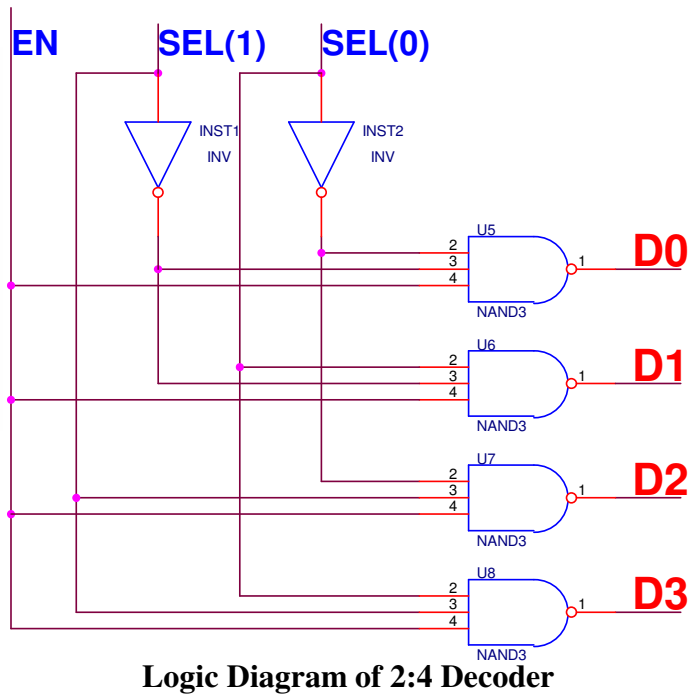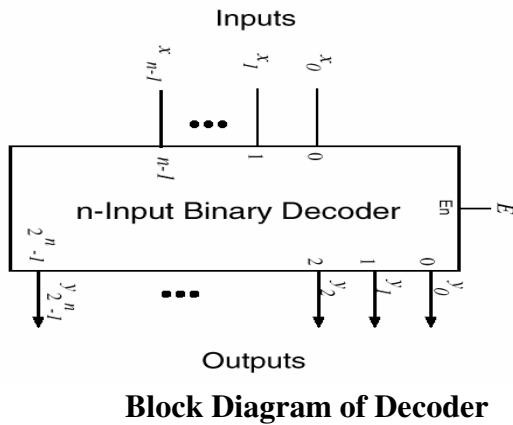- a) **2 to 4 decoder:** A decoder is a digital logic circuit that converts n-bits binary input code in to M output lines. **OR** It is a logic circuit that decodes from binary to octal, decimal, Hexa-decimal or any other code such as 7-segment etc.



EN	Inputs		Output
	Sel(1)	Sel(0)	D
1	X	X	0
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3

Truth table

VHDL LAB MANUAL

```
-----  
-- File           : decoder24.vhd  
-- Entity          : decoder24  
-----  
-- University      : Directorate of Technical Education, VLSI Design Lab V E&C  
-- Simulators      : Mentor Graphics Modelsim OR Active HDL  
-- Synthesizers    : Xilinx ISE  
-- Target Device   : Spartan II or XC Series  
-----  
-- Description     : 2 to 4 DECODER  
-----  
--The IEEE standard 1164 package, declares std_logic, etc.  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
----- Entity Declarations -----  
entity decoder24 is  
    generic(  
        N: INTEGER :=2;  
        M: INTEGER :=4 );  
    port (  
        EN : in STD_LOGIC;  
        SEL: in STD_LOGIC_VECTOR (N-1 downto 0);  
        D: out STD_LOGIC_VECTOR (M-1 downto 0) );  
end decoder24;  
architecture decoder24_arch of decoder24 is  
    signal aux: INTEGER;  
begin  
    aux<=conv_integer(SEL);  
    process(EN,aux)  
    begin  
        if (EN='1') then  
            for i in 0 to M-1 loop  
                if aux=i then  
                    D(i)<='1' ;  
                else  
                    D(i)<='0' ;  
                end if;  
            end loop;  
        end if;  
    end process;  
end decoder24_arch;
```

VHDL LAB MANUAL


```

                D(i)<='0' ;
            end if;
        end loop;
    else
        for i in 0 to M-1 loop
            D(i)<='0' ;
        end loop;
    end if;

end process;
end decoder24_arch;

```

Simulator Waveforms for 2:4 Decoder:

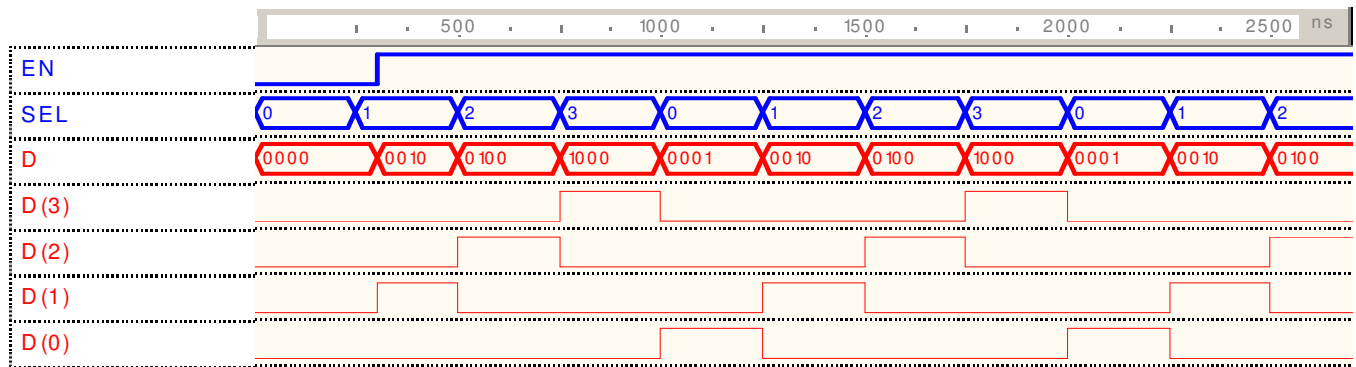

b) 8 to 3 (Encoder without & with priority)

Encoder: A logic circuit that produces coded binary outputs from uncoded inputs.


Priority encoder: Whenever two or more inputs are applied at a time, internal hardware will check this condition and if the priority is set such that higher numbered input should be taken into account and remaining are considered as don't care then output code will be appear will be "higher numbered input".

Truth table for 8-input priority encoder

EN	DIN (7:0)	EOUT
0	X X X X X X X X	0
1	X X X X X X X 0	0
1	X X X X X X 0 1	1
1	X X X X X 0 1 1	2
1	X X X X 0 1 1 1	3
1	X X X 0 1 1 1 1	4
1	X X 0 1 1 1 1 1	5

VHDL LAB MANUAL

1	X 0 1 1 1 1 1 1	6
1	0 1 1 1 1 1 1 1	7
1	1 1 1 1 1 1 1 1	0

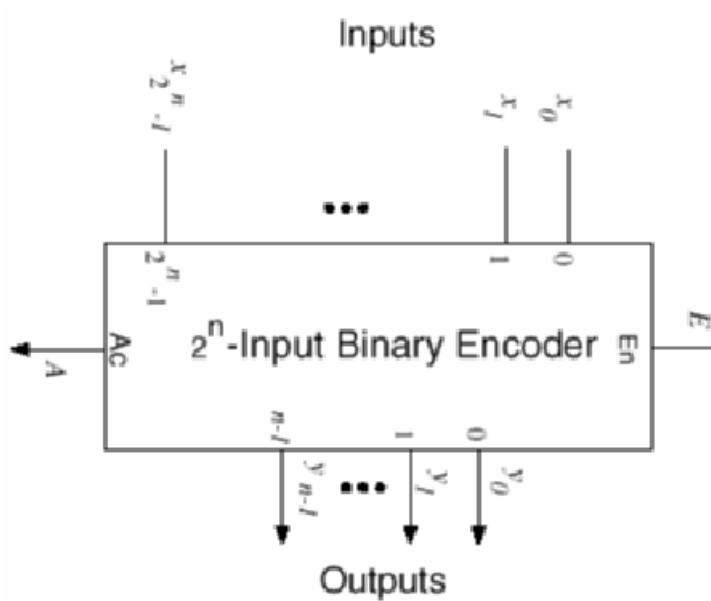

Block Diagram of priority encoder

```

-----
-- File      :      pencoder.vhd
-- Entity    :      pencoder
-----

-- University      : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators      :      Mentor Graphics Modelsim OR Active HDL
-- Synthesizers    :      Xilinx ISE
-- Target Device   :      Spartan II or XC Series
-----

-- Description    :      8-input priority encoder
-----

--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----
entity pencoder is
port (
    X: in STD_LOGIC_VECTOR (7 downto 0);

```


VHDL LAB MANUAL

```
E: in STD_LOGIC;  
Y: out STD_LOGIC_VECTOR (2 downto 0);  
A: out STD_LOGIC  
);  
end pencoder;
```



architecture pencoder_arch of pencoder is
begin

```
pe: process(x,E)  
variable k: integer;  
begin  
y <= "000";  
A <= '0';  
if E = '1' then  
for j in 0 to 7 loop  
if x(j) = '1' then  
y <= conv_std_logic_vector(j,3);  
A <= '1';  
end if;  
end loop;  
end if;  
end process pe;  
end pencoder_arch;
```

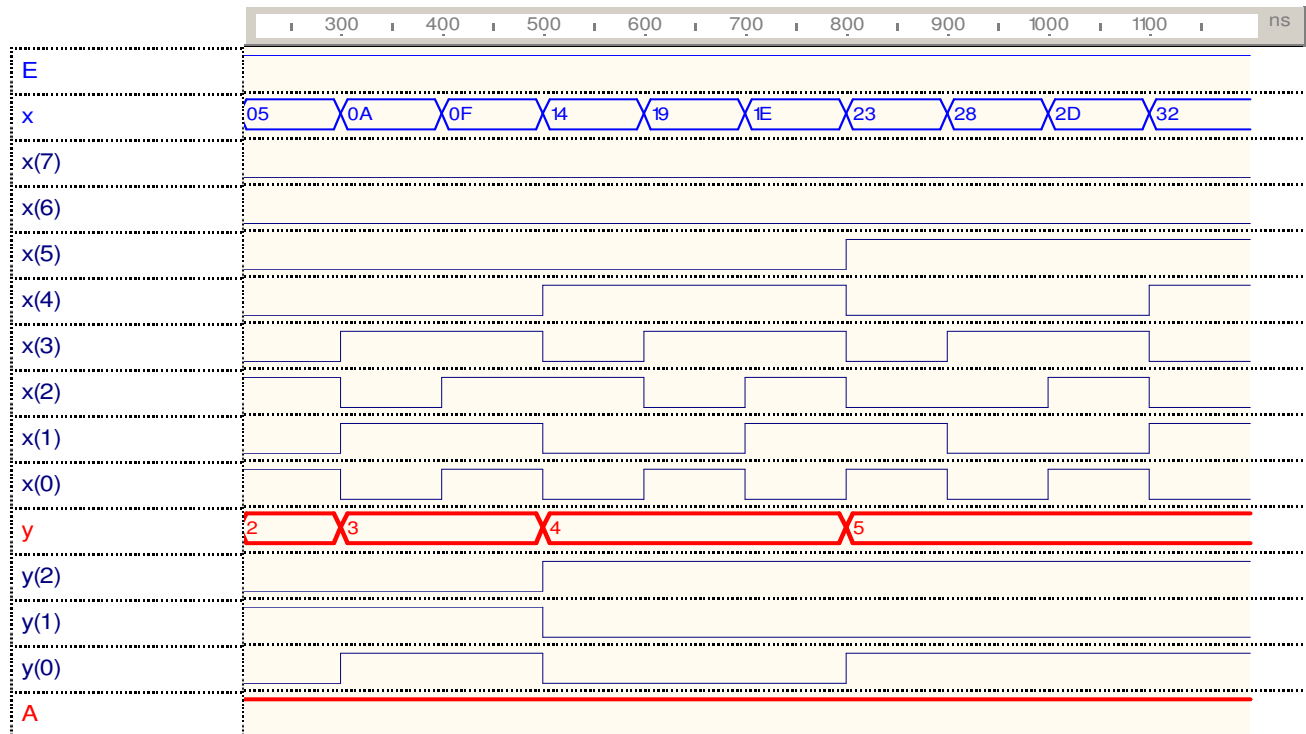Simulator Waveforms for 8-input priority encoder:



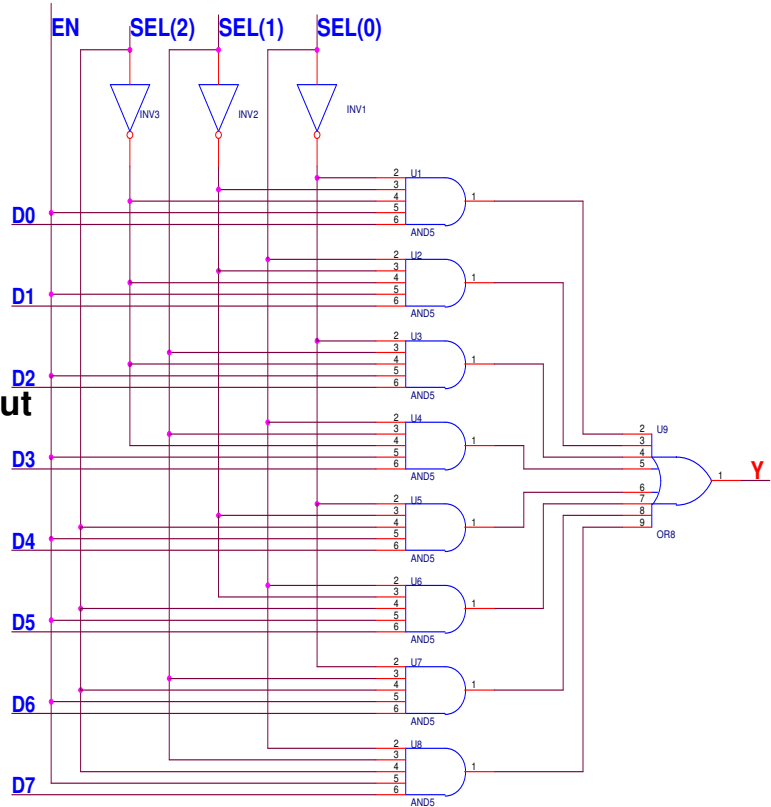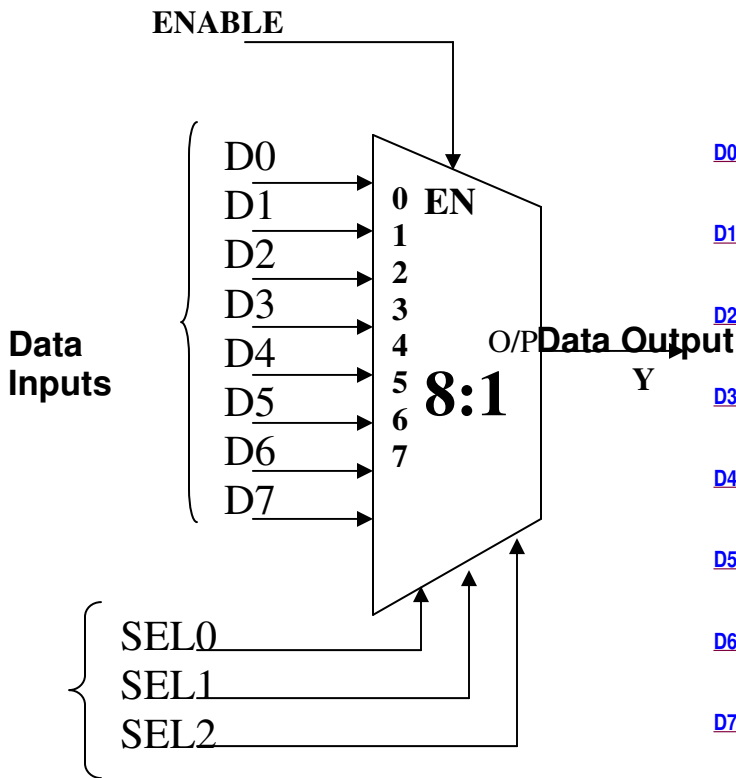c) **8 :1 Multiplexer**: The multiplexer is a combinational circuit which accepts several data inputs and allows only one of them AT A TIME to get through to the output.



Control Inputs
Block Diagram of 8:1 Mux

Logic Diagram

EN	CONTROL INPUTS			OUTPUT(Y) (Selected Inputs)
	SEL(3)	SEL(3)	SEL(3)	
0	0	0	0	D0
1	0	0	1	D1
1	0	1	0	D2
1	0	1	1	D3
1	1	0	0	D4
1	1	0	1	D5

VHDL LAB MANUAL

1	1	1	0	D6
1	1	1	1	D7

```
-----  
-- File           : mux8_1.vhd  
-- Entity          : mux8_1  
-----  
-- University      : Directorate of Technical Education, VLSI Design Lab V E&C  
-- Simulators      : Mentor Graphics Modelsim OR Active HDL  
-- Synthesizers    : Xilinx ISE  
-- Target Device   : Spartan II or XC Series  
-----  
-- Description     : 8 TO 1 MULTIPLEXOR  
-----
```

```
--The IEEE standard 1164 package, declares std_logic, etc.
```

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;
```

```
----- Entity Declarations -----
```

```
entity mux8_1 is  
    port (  
        D: in STD_LOGIC_VECTOR (7 downto 0);  
        EN: in STD_LOGIC;  
        SEL: in STD_LOGIC_VECTOR (2 downto 0);  
        Y: out STD_LOGIC );
```

```
end mux8_1;
```

```
architecture mux8_1_arch of mux8_1 is
```

```
begin
```

```
    process(EN,SEL,D)
```

```
    begin
```

```
        if(EN='1')then
```

```
            y<='0';
```

```
        else
```

```
            case SEL is
```

```
                when "000" => y <= D(0);
```

```
                when "001" => y <= D(1);
```

```
                when "010" => y <= D(2);
```

```
                when "011" => y <= D(3);
```

```
                when "100" => y <= D(4);
```

```
                when "101" => y <= D(5);
```

```
                when "110" => y <= D(6);
```

```
                when others=> y <= D(7);
```


```
            end case;
```

```

        end if;
    end process;

end mux8_1_arch;
    
```

Simulator Waveforms for 8:1 Multiplexer:

 


d) 4-bit Binary to Gray converter.

Binary –It is a number system, which has only two states ‘0’ (high) and ‘1’ (low)

Gray- In Gray code “ Every new code differs from the previous in terms of single bit” only one bit changes between successive numbers.

Decimal	Binary	Gray
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101
10	1010	1111

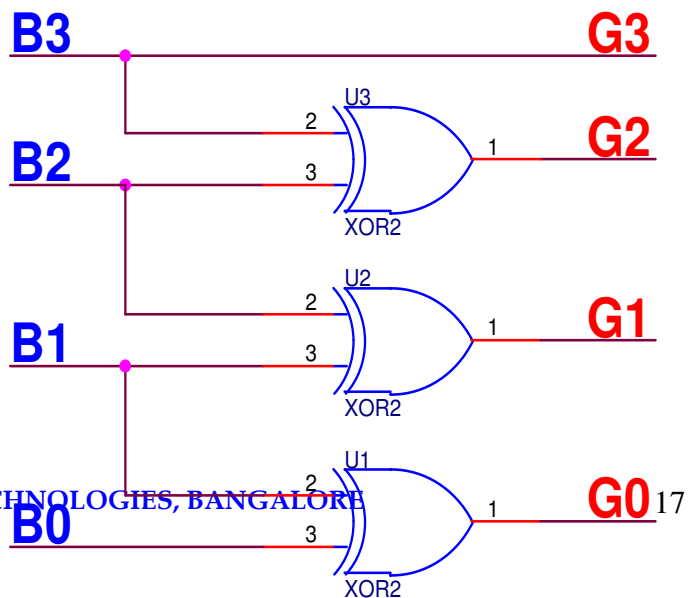

VHDL LAB MANUAL

11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

```
-----  
-- File           :b2g.vhd  
-- Entity        :b2g  
-----  
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C  
-- Simulators     :      Mentor Graphics Modelsim OR Active HDL  
-- Synthesizers   :      Xilinx ISE  
-- Target Device  :      Spartan II or XC Series  
-----  
-- Description    :      4-BIT BINARY TO GRAY CONVERTOR  
-----
```

```
--The IEEE standard 1164 package, declares std_logic, etc.  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;
```


```
----- Entity Declarations -----  
entity b2g is  
  port (  
    B3,B2,B1,B0: in STD_LOGIC;  
    G3,G2,G1,G0: out STD_LOGIC  
  );  
end b2g;
```

```
architecture b2g_arch of b2g is
```

```
begin  
  G3<=B3;  
  G2<=B2 xor B3;  
  G1<=B1 xor B2;  
  G0<=B0 xor B1;
```

```
end b2g_arch;
```

 
Simulator Waveforms for 4-Bit Binary to Gray Conversion:



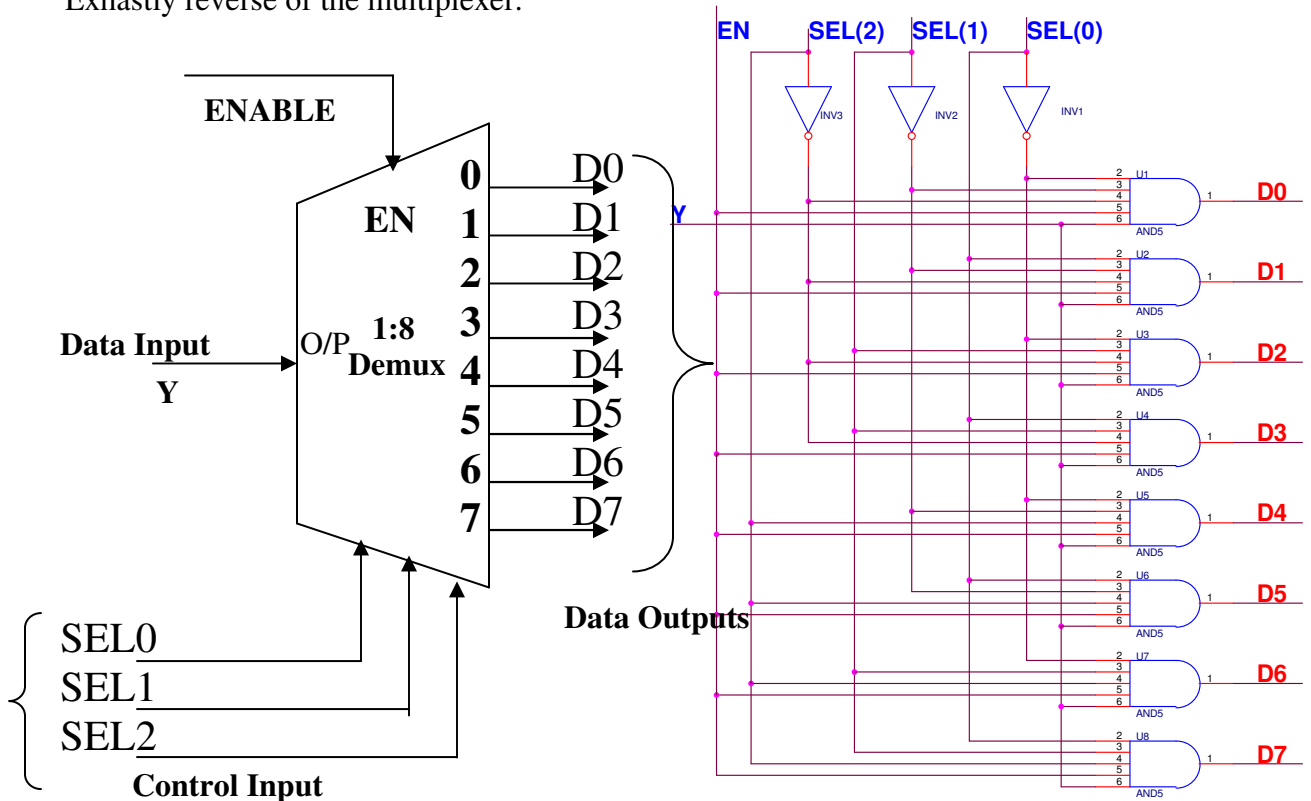e) Multiplexer, Demultiplexer, comparator.

Multiplexer: Ref Exp 2(b)

Demultiplexer: Demultiplexer is a combinational circuit that accepts single input and distributes it several outputs (Selectively distributes it to 1 of N output channels) & Exhastly reverse of the multiplexer.



Block Diagram of 1:8 Demux

Logic Diagram

Truth Table

EN	CONTROL INPUTS			OUTPUTS
	SEL(3)	SEL(3)	SEL(3)	
0	X	X	X	0
1	0	0	0	D0=Y
1	0	0	1	D1=Y
1	0	1	0	D2=Y
1	0	1	1	D3=Y
1	1	0	0	D4=Y

VHDL LAB MANUAL

1	1	0	1	D5=Y
1	1	1	0	D6=Y
1	1	1	1	D7=Y

```
-----  
-- File           : demux.vhd  
-- Entity         : demux  
-----  
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C  
-- Simulators     : Mentor Graphics Modelsim OR Active HDL  
-- Synthesizers   : Xilinx ISE  
-- Target Device  : Spartan II or XC Series  
-----  
-- Description    : 1:8 DEMULTIPLEXOR  
-----  
--The IEEE standard 1164 package, declares std_logic, etc.  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
----- Entity Declarations -----  
entity demux8_1 is  
    port ( Y      : in STD_LOGIC;  
          EN      : in STD_LOGIC;  
          SEL     : in STD_LOGIC_VECTOR (2 downto 0);  
          D       : out STD_LOGIC_VECTOR (7 downto 0) );  
end demux8_1;  
  
architecture demux8_1_arch of demux8_1 is  
begin  
    process(EN,SEL,Y)  
    begin  
        if(EN='1')then  
            D<=(others=>'0');  
        else  
            case SEL is  
                when "000" => D(0)<=Y;  
                when "001" => D(1)<=Y;  
                when "010" => D(2)<=Y;  
                when "011" => D(3)<=Y;  
                when "100" => D(4)<=Y;  
                when "101" => D(5)<=Y;  
                when "110" => D(6)<=Y;  
                when others=> D(7)<=Y;  
            end case;  
        end process;  
    end architecture;
```


```

end if;
end process;

end demux8_1_arch;

```

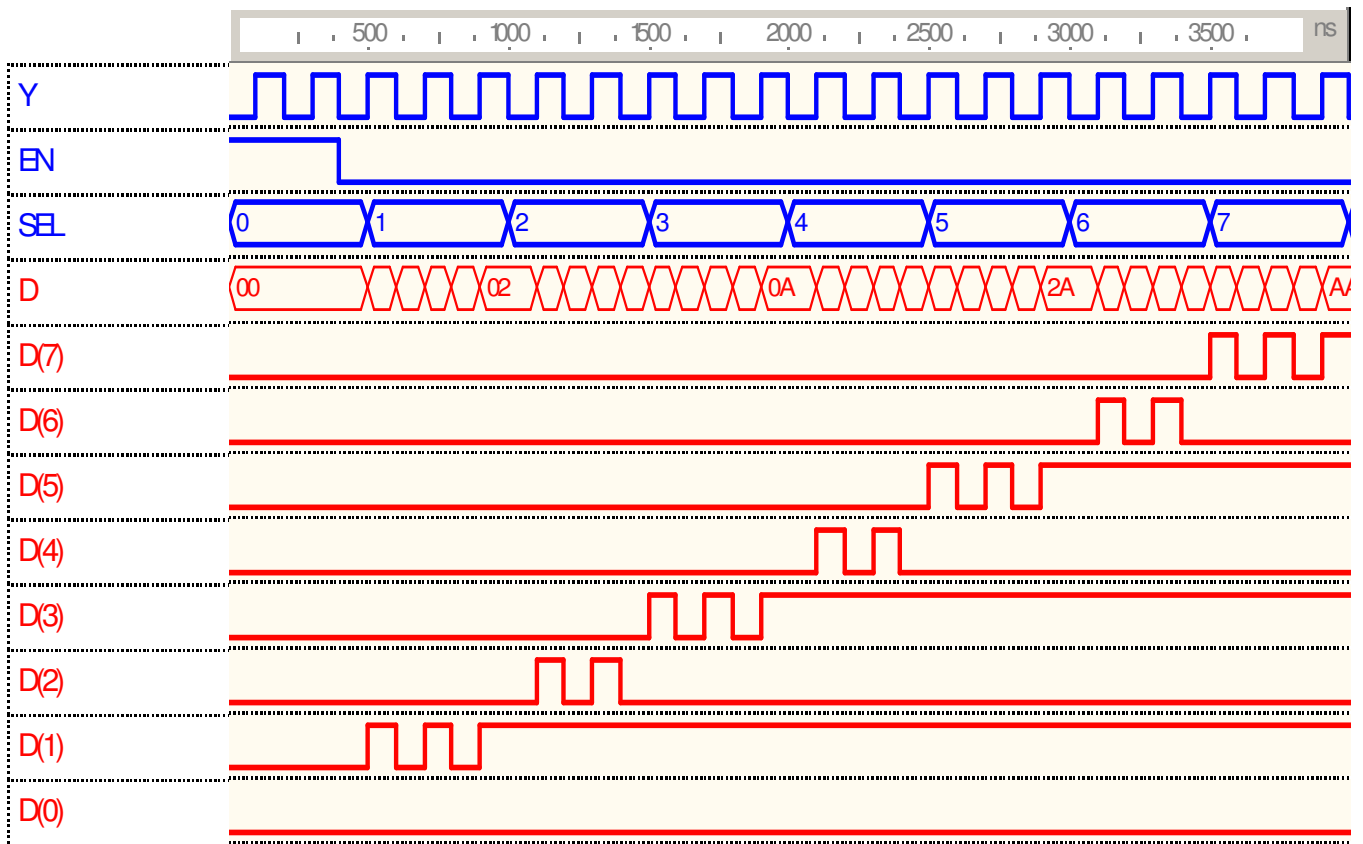Simulator Waveforms for 1: Demultiplexer:




Comparator: A circuit that compares two numbers and produces an output indicating whether they are equal. It may also indicate which number is greater if they are unequal. Ex: '1' bit comparator

Truth table:

Comparing inputs		Outputs		
A	B	$Y=(A>B)$	$Y=(A<B)$	$Y=(A=B)$
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1


:

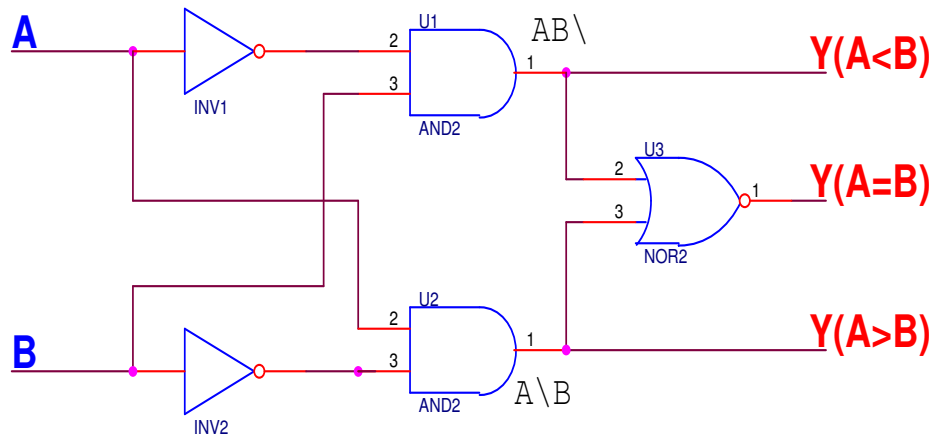

VHDL LAB MANUAL

```
-----  
-- File           : bitcomp.vhd  
-- Entity         : bitcomp  
-----  
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C  
-- Simulators     : Mentor Graphics Modelsim OR Active HDL  
-- Synthesizers   : Xilinx ISE  
-- Target Device  : Spartan II or XC Series  
-----  
-- Description    : SINGLE BIT MAGNITUDE COMPARATOR.  
-----  
  
--The IEEE standard 1164 package, declares std_logic, etc.  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
----- Entity Declarations -----  
entity bitcomp is  
    port (  
        A: in STD_LOGIC;  
        B: in STD_LOGIC;  
        sel: in STD_LOGIC_VECTOR(1 DOWNTO 0);  
        Y: out BOOLEAN  
    );  
end bitcomp;  
  
architecture bitcomp_arch of bitcomp is  
begin  
    process(A,B,sel)  
    begin  
        case sel is  
            when "00" => y <= A=B;  
            when "01" => y <= A>B;  
            when "10" => y <= A<B;  
            when others => y <= FALSE ;  
        end case;  
    end process;  
end bitcomp_arch;
```


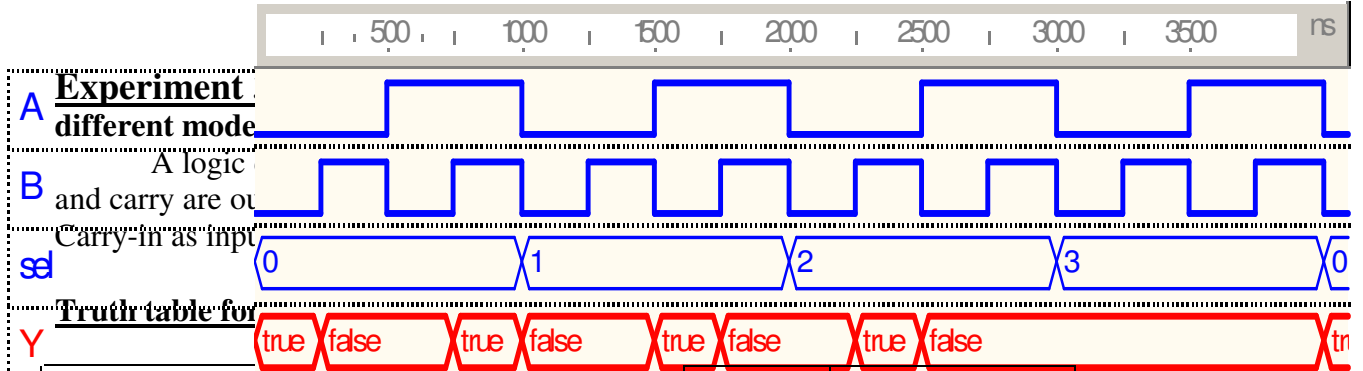
Simulator Waveforms for SINGLE BIT MAGNITUDE COMPARATOR:




Truth table for

INPUTS			OUTPUTS	
A	B	Cin	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

INPUTS		OUTPUTS	
A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 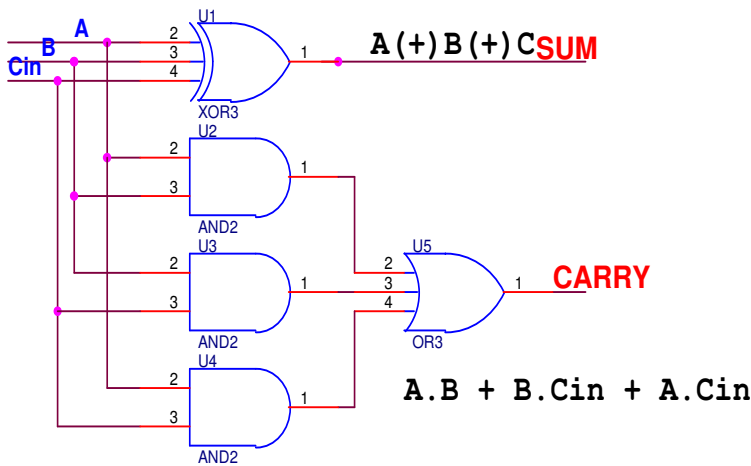

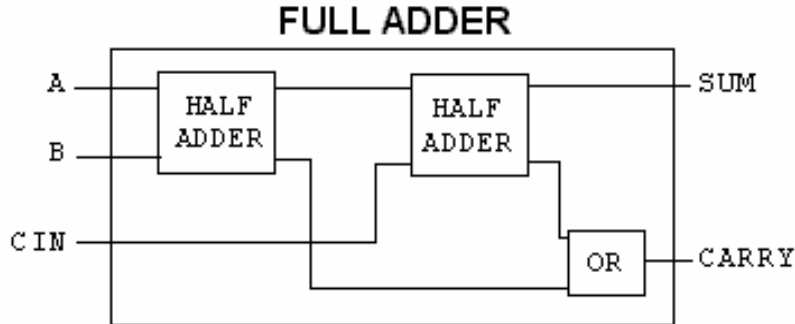

Full adder using 2-Half adder

VHDL Code for HALF ADDER

```

-- File           : HA.vhd
-- Entity         : HA
-- Architecture   : HA_arch
-----
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     : Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   : Xilinx ISE
-- Target Device  : Spartan II or XC Series
-----
-- Description    : HALF ADDER.
-----

--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----

entity HA is
    port(
        A,B : in STD_LOGIC;
        S,CY : out STD_LOGIC
    );
end HA;

architecture HA_arch of HA is
begin
    S<= A XOR B;
    CY<= A AND B;

```

end HA_arch;

VHDL Code for FULL ADDER

-- *STRUCTURAL MODELING-A set of interconnect with different COMPONENT*

```
-- File           : FA.vhd
-- Entity         : FA
-- Architecture   : FA_arch
```

```
-----
-- University    : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators    : Mentor Graphics Modelsim OR Active HDL
-- Synthesizers  : Xilinx ISE
-- Target Device : Spartan II or XC Series
-----
```

```
-- Description   : FULL ADDER.
-----
```

--The IEEE standard 1164 package, declares std_logic, etc.

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
```

----- Entity Declarations -----

```
entity FA is
    port(
        A,B,Cin : in STD_LOGIC;
        SUM,CARRY : out STD_LOGIC
    );
end FA;
```

architecture STRUCTURAL of FA is

```
    signal sum1,cy1,cy2:std_logic;
    component HA
        port(
            A,B : in STD_LOGIC;
            S,CY : out STD_LOGIC
        );
    end component ;
begin
    u1: HA port map(A=>A, B=>B, S=>SUM1, CY=>CY1);
    u2: HA port map(A=>SUM1, B=>Cin, S=>SUM, CY=>CY2);

    CARRY<= cy1 OR cy2;
```

VHDL LAB MANUAL

end STRUCTURAL;

-- **DATAFLOW MODELING**- *A set of concurrent assignment statements.*

architecture DATAFLOW of FA is

begin

```
SUM<= A XOR B XOR Cin;  
CARRY<= (A AND B) OR (Cin AND A)OR (Cin AND B);
```

end DATAFLOW;

-- **BEHAVIORAL MODELING**-*A set of sequential assignment statements according to the behavior of the design. (Process is single concurrent statement, which has sequential statements.)*


architecture BEHAVIOR of FA is

begin


```
process(A,B,Cin)  
begin  
    SUM<= A XOR B XOR Cin;  
    CARRY<= (A AND B) OR (Cin AND A)OR (Cin AND B);  
end process;
```

end BEHAVIOR;

Simulator waveforms of HALF ADDER

 

Simulator waveforms of FULL ADDER

 

**Experiment 4: Write a model for 32 bit ALU using the schematic diagram
Shown below example**

- ALU should use the combinational logic to calculate an output based on the four bit Opcode input.
- ALU should pass the result to the out bit when enable line is high and tri-state when low enable.
- ALU should decode the 4-bit op-code according to the given in example below

Opcode	ALU operation
1	A + B
2	A – B
3	A Complement
4	A * B
5	A AND B
6	A OR B
7	A NAND B
8	A XOR B

Function table for ALU


<u>Enable</u>	<u>Mode</u>	<u>Opcode</u>	<u>Functional description</u>
0	X	XXXX	Y<="Z" (Tri-stated)
1	0	0001	Y<= A + B ;
1	0	0010	Y<= A – B;
1	0	0011	Y <= A(15:0)* B(15:0)* ;
1	1	0100	Y <= NOT A (Complement)
1	1	0101	Y <= A AND B (AND Operation)
1	1	0110	Y <= A OR B (OR Operation)
1	1	0111	Y <= A NAND B (NAND Operation)
1	1	1000	Y <= A XOR B (XOR Operation)
1	X	1001	Y <= Y (ALU is ideal or previous data is

VHDL LAB MANUAL

			latched for all other higher opcodes.
1	X	1010	“ “
1	X	1011	“ “
1	X	1100	“ “
1	X	1101	“ “
1	X	1110	“ “
1	X	1111	“ “

ARTHAMETIC LOGIC UNIT (ALU)

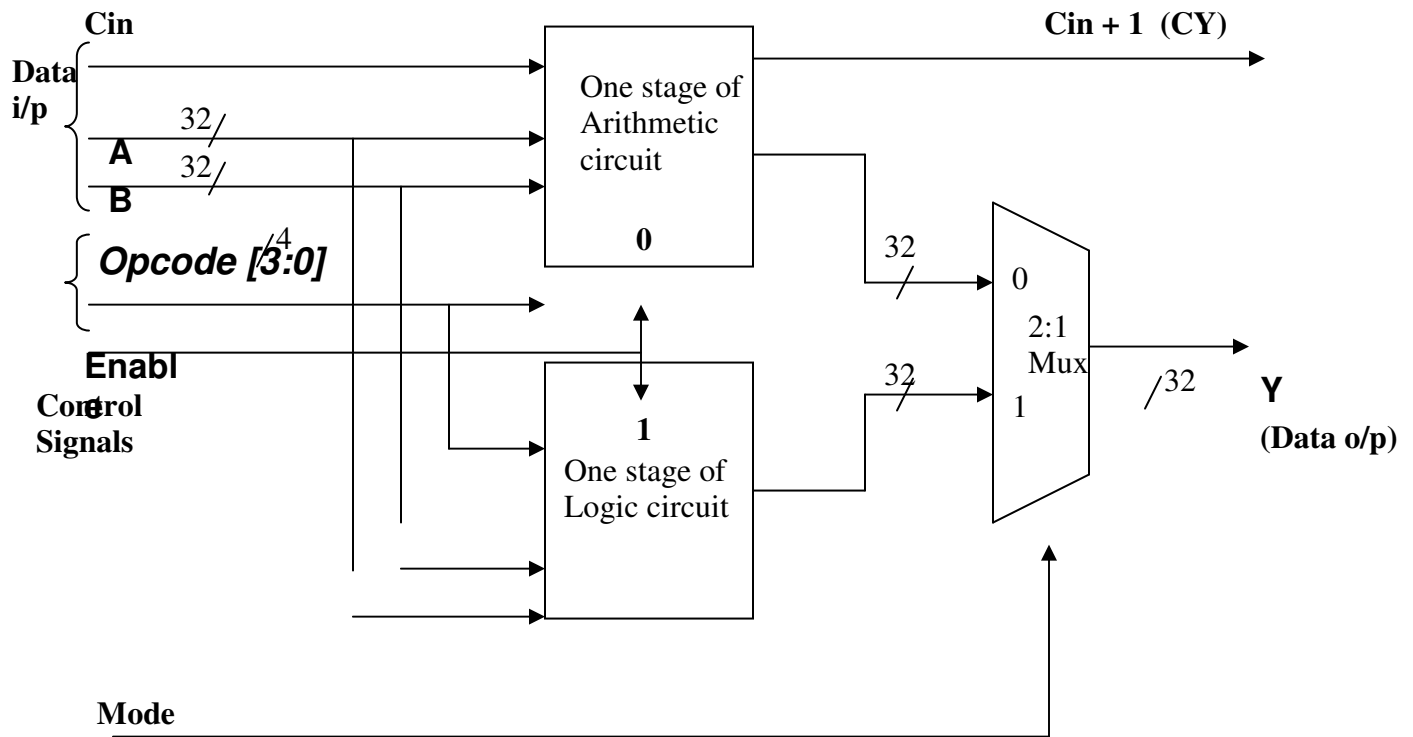ALU is logic circuit which is able to perform different arithmetic and logical function basically ALU is the heart of central processing unit (CPU).



Mode : '0' ___ Arthmatic operation
 '1' ___ Logic operation

VHDL LAB MANUAL

Enable '0' → Y <= " Z "
'1' → Out put performed

Note: For A*B, A&B lower 16 bit [15:0] can be taken in to consideration.

VHDL Code for 8 bit ALU:

```
-- File           :   alu.vhd
-- Entity         :   alu
-----
-- University     :   Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     :   Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   :   Xilinx ISE
-- Target Device  :   Spartan II or XC Series
-----
-- Description    :   8-bit ALU.
-----
--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.Std_Logic_1164.all;
use IEEE.NUMERIC_STD.all;
----- Entity Declarations -----
--      NOTE : JUST BY CHANGING THE WIDTH OF INPUT AND OUTPUT
--      OF (31 DOWNT0 O)
--      WILL BECOME 32-BIT ALU
-----
entity Alu is
    port( Clk   : in  Std_Logic;
          MODE,EN: in  Std_Logic;
          A,B   : in  Std_Logic_Vector(7 downto 0);
          OPCODE : in  Std_Logic_Vector(3 downto 0);
          Y     : out Std_Logic_Vector(7 downto 0));
end Alu;

architecture Alu_a of Alu is
    signal C_s : Unsigned(7 downto 0);
begin

    process (A, B,OPCODE,mode)
        variable A_v : Unsigned(7 downto 0);
        variable B_v : Unsigned(7 downto 0);
    begin
        A_v := Unsigned(A);
        B_v := Unsigned(B);
        if(EN='0')then
            C_s<=(others=>'Z');
            if(mode='0')then
                case OPCODE is
```

VHDL LAB MANUAL


```

                                when "0000" => C_s <= A_v + B_v;
                                when "0001" => C_s <= A_v - B_v;
when "0010" => C_s <= A_v(3 downto 0) * B_v(3 downto 0);
when others => C_s <= (others => '0');
end case;
    else
        case opcode is
            when "0011" => C_s <= not A_v;
            when "0100" => C_s <= not B_v;
            when "0101" => C_s <= A_v and B_v;
            when "0110" => C_s <= A_v nand B_v;
            when "0111" => C_s <= A_v or B_v;
            when "1000" => C_s <= A_v nor B_v;
            when "1001" => C_s <= A_v xor B_v;
            when "1010" => C_s <= A_v xnor B_v;
            when others => C_s <= (others => '0');
        end case;
    end if;
end if;
end process;

process
begin
    wait until Clk'event and Clk = '1';
    y <= Std_Logic_Vector(C_s);
end process ;
end Alu_a;


```

Simulator waveforms for 8 bit ALU:

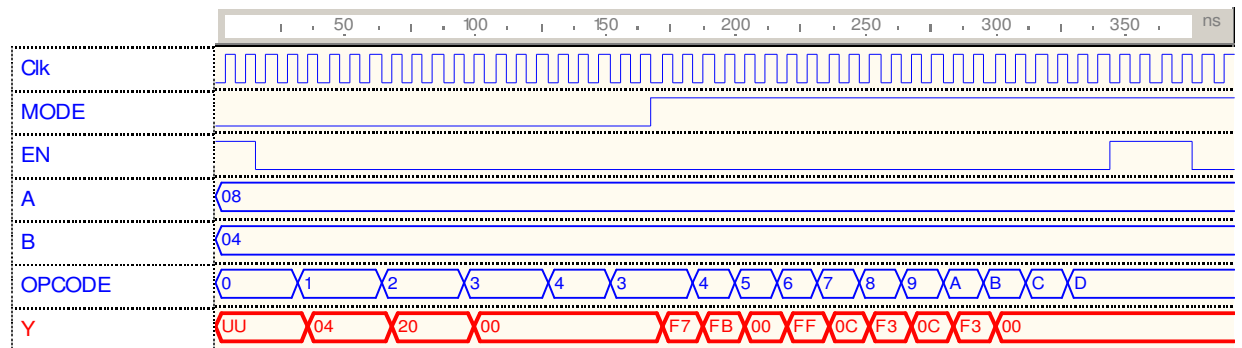


Experiment 5: Develop the VHDL code for the following flip-flops SR, D, JK & T.

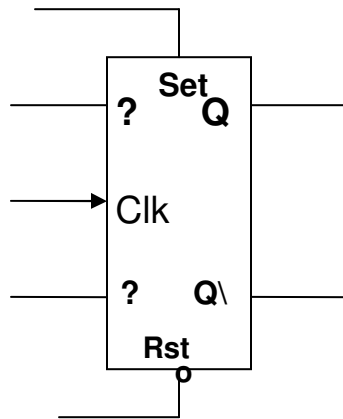Flip-flop: Flip-flop is a sequential logic circuit, which is 'One'-bit memory element. OR It is a basic memory element in digital systems (same as the bi-stable multivibrator) It has two stable state logic '1' and logic '0'.



Positive
Edge-Triggered

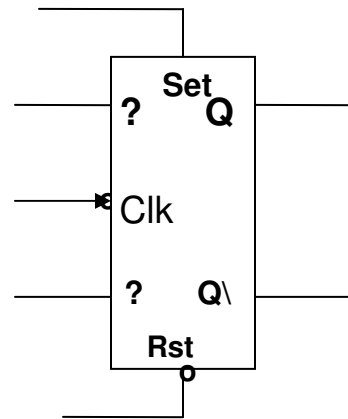

Negative Edge-Triggered

(a) S-R Flip-flop (Set-Reset)

VHDL LAB MANUAL

In a memory device set and Reset is often required for synchronization of the device in such case S-R Flip-flop is need & this is refereed as clocked set-reset.

◆ Set-Reset Truth table

S	R	Q ⁺	Action
0	0	Q	No Change
0	1	0	Reset
1	0	1	Set
1	1	-	Illegal


VHDL Code for SR Flip-Flop:

```
-----  
-- File           : SRFF.vhd  
-- Entity        : SRFF  
-----  
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C  
-- Simulators     : Mentor Graphics Modelsim OR Active HDL  
-- Synthesizers  : Xilinx ISE  
-- Target Device  : Spartan II or XC Series  
-----  
-- Description    : SR Flip-Flop  
-----  
--The IEEE standard 1164 package, declares std_logic, etc.  
  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
----- Entity Declarations -----  
entity SRFF is  
    port (  
        CLK, RST, S, R : in std_logic;
```

VHDL LAB MANUAL

```
        Q, Qn      : out std_logic);
end SRFF;
architecture RTL of SRFF is
    signal FF : std_logic;
begin
    process (CLK, RST)
        variable SR : std_logic_vector(1 downto 0);
    begin
        if (RST = '0') then
            FF <= '0';
        elsif (CLK'event and CLK = '1') then
            SR := S & R;
            case SR is
                when "01" => FF <= '0';
                when "10" => FF <= '1';
                when "11" => FF <= 'Z';
                when others => FF <= FF;
            end case;
        end if;
    end process;
    Q <= FF ;
    Qn <= not FF ;
end RTL;
```

Simulator waveforms for SR Flip-Flop:

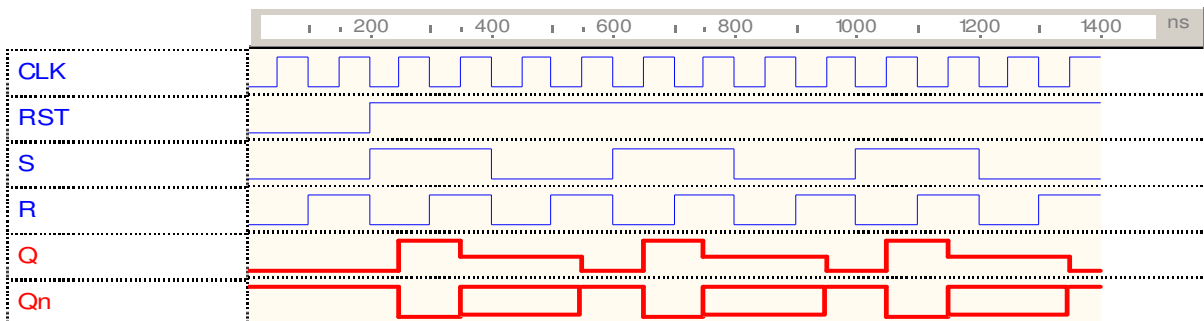

(b) D- FF (Delay Flip-flop)

(c)

In D-Flip-flop the transfer of data from the input to the Output is delayed and hence the name delay D-Flip-flop. The D-Type Flip-flop is either used as a delay device or as a latch to store '1' bit of binary information.

D input transferred to Q output when clock asserted

D-F/F Truth table

D	Q ⁺	Action
0	0	Reset
1	1	Set

Note: - D is used to avoid the possibility of race condition in SR flip flop.
 - The Output = Input when clock is applied.

VHDL Code for D Flip-Flop:

```

-----
-- File           : DFF.vhd
-- Entity         : DFF
-----
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     : Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   : Xilinx ISE
-- Target Device  : Spartan II or XC Series
-----
-- Description    : D Flip-Flop
-----
--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----
entity dff is
    port (data, clk, reset : in std_logic;
          Q,QB : out std_logic);
end dff;

architecture behav of dff is
begin
    process (clk, reset) begin
        if (reset = '1') then
            Q <= '0';


```

```

        QB <= '1';
    elsif (clk'event and clk = '1') then
        Q <= data;
        QB<= not data;
    end if;
end process;
end behav;

```

Simulator waveforms for D Flip-Flop

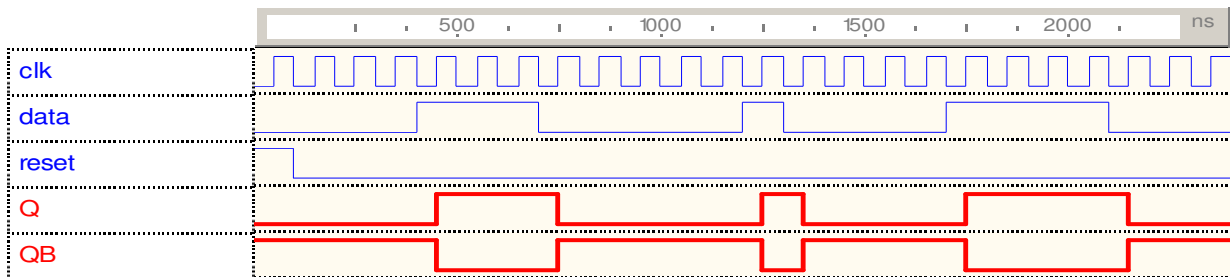

c) J.K Flip-flop:

The race conditions in S-R Flip-flop can be eliminated by converting it in to J.K, the data inputs J and K are ANDED with Q\ and Q to obtain S & R inputs.

Here **SR, T, or D depending on inputs.**

$$S=J.Q'$$

$$R=K.Q$$

Logic diagram:

JK-F/F Truth table

J	K	Q ⁺	Action
0	0	Q	No Change
0	1	0	Reset
1	0	1	Set
1	1	Q'	Toggle

VHDL Code for JK Flip-Flop:


```

-----
-- File           : JKFF.vhd
-- Entity         : JKFF
-----
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     : Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   : Xilinx ISE
-- Target Device  : Spartan II or XC Series
-----
-- Description    :JK Flip-Flop
-----
--The IEEE standard 1164 package, declares std_logic, etc.

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----
entity JKFF is
    port (
        CLK, RST, J, K : in std_logic;
        Q, Qn          : out std_logic);
end JKFF;
architecture RTL of JKFF is
    signal FF : std_logic;
begin
    process (CLK, RST)
        variable JK : std_logic_vector(1 downto 0);
    begin
        if (RST = '0') then
            FF <= '0';
        elsif (CLK'event and CLK = '1') then
            JK := J & K;
            case JK is
                when "01" => FF <= '0';
                when "10" => FF <= '1';
                when "11" => FF <= not FF;
                when others => FF <= FF;
            end case;
        end if;
    end process;
    Q <= FF ;
    Qn <= not FF ;
end RTL;

```

Simulator waveforms for JK Flip-Flop

 

- d) **T-Flip-flop (Toggle Flip-flop):** On every change in clock pulse the output ‘Q’ changes its state (Toggle). A Flip-flop with one data input which changes state for every clock pulse.(J=K=’1’ in JQK Flip-flop the resulting output is ‘T’ Flip-flop).

T-F/F Truth table

T	Q ⁺	Action
0	Q	No Change
1	Q	Toggle

VHDL Code for T Flip-Flop:

```

-----
-- File           :      TFF.vhd
-- Entity         :      TFF
-----
-- University     :      Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     :      Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   :      Xilinx ISE
-- Target Device  :      Spartan II or XC Series
-----
-- Description    :      T Flip-Flop
-----
--The IEEE standard 1164 package, declares std_logic, etc.

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----


```

VHDL LAB MANUAL


```
entity tff is
    port (T, CLK, RST : in std_logic;
          Q,QB : out std_logic);
end tff;

architecture behav of tff is
begin
    process (clk, RST) begin
        if (RST = '1') then
            Q <= '1';
            QB <= '0';
        elsif (clk'event and clk = '1') then
            QB <= T;
            Q <= not T;
        end if;
    end process;
end behav;
```

Simulator waveforms for D Flip-Flop:

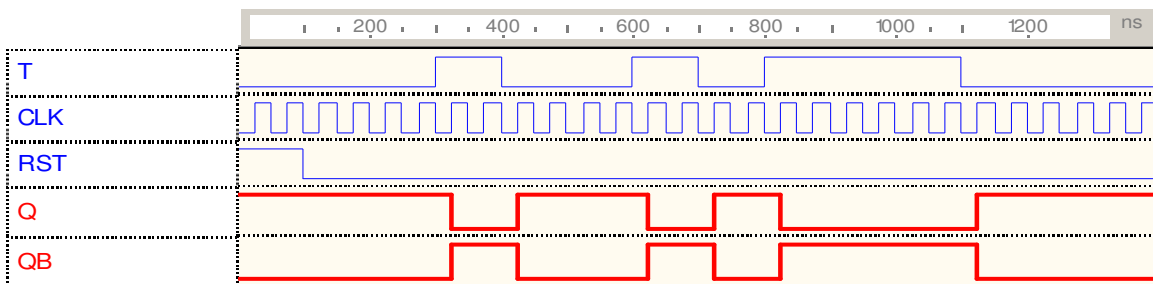

Gate level Example:

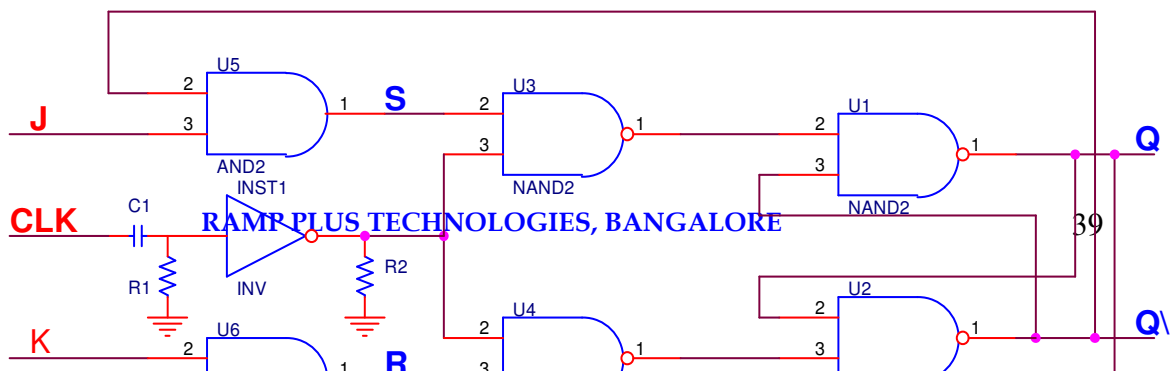


Experiment 6: Design 4-bit binary, BCD counters and any sequence counter
(With Synchronous /Asynchronous Reset).


COUNTER: Counter is a digital circuit that can counts the member of pulse for building the counters, Flip-flop are used.

Relation between number of Flip-flop used and number of state of counter is (Regular/binary counter).

Synchronous Counter:

 

Ripple Counter/Asynchronous Counter:

 

4-bit Binary counter (Synchronous counter)

```

-----
-- File           :   sync_rst_binary.vhd
-- Entity         :   sync_rst_binary
-- Architecture   :   sync_rst_binary_arch
-----

-- University    :   Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     :   Mentor Graphics Modelsim OR Active HDL
-- Synthesizers  :   Xilinx ISE
-- Target Device  :   Spartan II or XC Series
-----

-- Description   :   N-bit binary Up counter with synchronous reset
-----

--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----
entity sync_rst_binary is
    generic(N: INTEGER := 4);
    port(
        clock : in STD_LOGIC;
        reset  : in STD_LOGIC;
        qout  : out STD_LOGIC_VECTOR(N-1 downto 0)
    );
end sync_rst_binary;

architecture sync_rst_binary_arch of sync_rst_binary is
    signal temp_count: std_logic_vector(N-1 downto 0);
begin
    process(clock,reset)
    begin
        if(clock='1' and clock'event)then
            if(reset='1')then
                temp_count<=(others=>'0');
            else
                temp_count<= temp_count + 1;
            end if;
        end if;
    end process;
end sync_rst_binary_arch;

```

```

end process;
qout<=temp_count;
end sync_rst_binary_arch;

```

4-bit Binary up counter (Asynchronous counter)

```

-----
-- File           :      async_rst_binary.vhd
-- Entity         :      async_rst_binary
-- Architecture   :      async_rst_binary_arch
-----
-- University     :      Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     :      Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   :      Xilinx ISE
-- Target Device  :      Spartan II or XC Series
-----

```

```

-- Description :      N-bit binary Up counter with Asynchronous reset
-----

```

```

--The IEEE standard 1164 package, declares std_logic, etc.

```

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;

```

```

----- Entity Declarations -----

```

```

entity async_rst_binary is
    generic(N: INTEGER := 4);
    port(
        clock : in STD_LOGIC;
        reset  : in STD_LOGIC;
        qout   : out STD_LOGIC_VECTOR(N-1 downto 0)
    );
end async_rst_binary;

```

```

architecture async_rst_binary_arch of async_rst_binary is
    signal temp_count: std_logic_vector(N-1 downto 0);

```

```

begin
    process(clock,reset)
    begin
        if(reset='1')then
            temp_count<=(others=>'0');
        elsif(clock='1' and clock'event)then
            temp_count<= temp_count + 1;
        end if;
    end process;
    qout<=temp_count;
end async_rst_binary_arch;

```

4-bit BCD up counter (Synchronous counter)

```

-----
-- File           : sync_rst_BCD.vhd
-- Entity         : sync_rst_BCD
-- Architecture   : sync_rst_BCD_arch
-----

-- University     : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     : Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   : Xilinx ISE
-- Target Device  : Spartan II or XC Series
-----

-- Description    : N-bit BCD UP counter with Synchronous reset
-----

--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----
entity sync_rst_BCD4 is
    generic(N: INTEGER := 4);
    port(
        clock : in STD_LOGIC;
        reset  : in STD_LOGIC;
        qout  : out STD_LOGIC_VECTOR(N-1 downto 0)
    );
end sync_rst_BCD4;

architecture sync_rst_BCD4_arch of sync_rst_BCD4 is
    signal temp_count: std_logic_vector(N-1 downto 0);
begin
    process(clock,reset)
    begin
        if (clock='1' and clock'event)then
            if(reset='1')then
                temp_count<=(others=>'0');
            else
                temp_count<= temp_count + 1;
                if(temp_count="1001")then
                    temp_count<=(others=>'0');
                end if;
            end if;
        end if;
    end process;
    qout<=temp_count;
end sync_rst_BCD4_arch;

```

4-bit BCD up counter (Asynchronous Reset)

```

-----
-- File           :   async_rst_BCD.vhd
-- Entity         :   async_rst_BCD
-- Architecture   :   async_rst_BCD_arch
-----

-- University     :   Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     :   Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   :   Xilinx ISE
-- Target Device  :   Spartan II or XC Series
-----

-- Description    :   N-bit BCD UP counter with Aynchronous reset
-----

--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----
entity async_rst_BCD4 is
    generic(N: INTEGER := 4);
    port(
        clock : in STD_LOGIC;
        reset  : in STD_LOGIC;
        qout   : out STD_LOGIC_VECTOR(N-1 downto 0)
    );
end async_rst_BCD4;

architecture async_rst_BCD4_arch of async_rst_BCD4 is
    signal temp_count: std_logic_vector(N-1 downto 0);
begin
    process(clock,reset)
    begin
        if(reset='1')then
            temp_count<=(others=>'0');
        elsif(clock='1' and clock'event)then
            temp_count<= temp_count + 1;
            if(temp_count="1001")then
                temp_count<=(others=>'0');
            end if;
        end if;
    end process;
    qout<=temp_count;
end async_rst_BCD4_arch;

```

4-bit Gray up counter (Asynchronous Reset)


```

-----
-- File           :   graycnt.vhd
-- Entity         :   graycnt
-- Architecture   :   graycnt_arch
-----
-- University     :   Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     :   Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   :   Xilinx ISE
-- Target Device  :   Spartan II or XC Series
-----
-- Description    :   N-bit Gary up counter with Asynchronous reset
-----
--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;
----- Entity Declarations -----
entity graycnt is
    generic(N: INTEGER := 4);
    port(
        clock : in STD_LOGIC;
        reset  : in STD_LOGIC;
        grayout,binaryout : out std_logic_vector(N-1 downto 0)
    );
end graycnt;
architecture graycnt of graycnt is
    signal temp_count: std_logic_vector(N-1 downto 0);
begin
    process(clock,reset)
    begin
        if(reset='1')then
            temp_count<=(others=>'0');
        elsif(clock='1' and clock'event)then
            temp_count<= temp_count + 1;
        end if;
    end process;
    binaryout<=temp_count;
    grayout(3)<=temp_count(3);
    grayout(2)<=temp_count(3)xor temp_count(2);
    grayout(1)<=temp_count(2)xor temp_count(1);
    grayout(0)<=temp_count(1)xor temp_count(0);


end graycnt;

```


Waveforms for 4-Bit Binary Up Counter

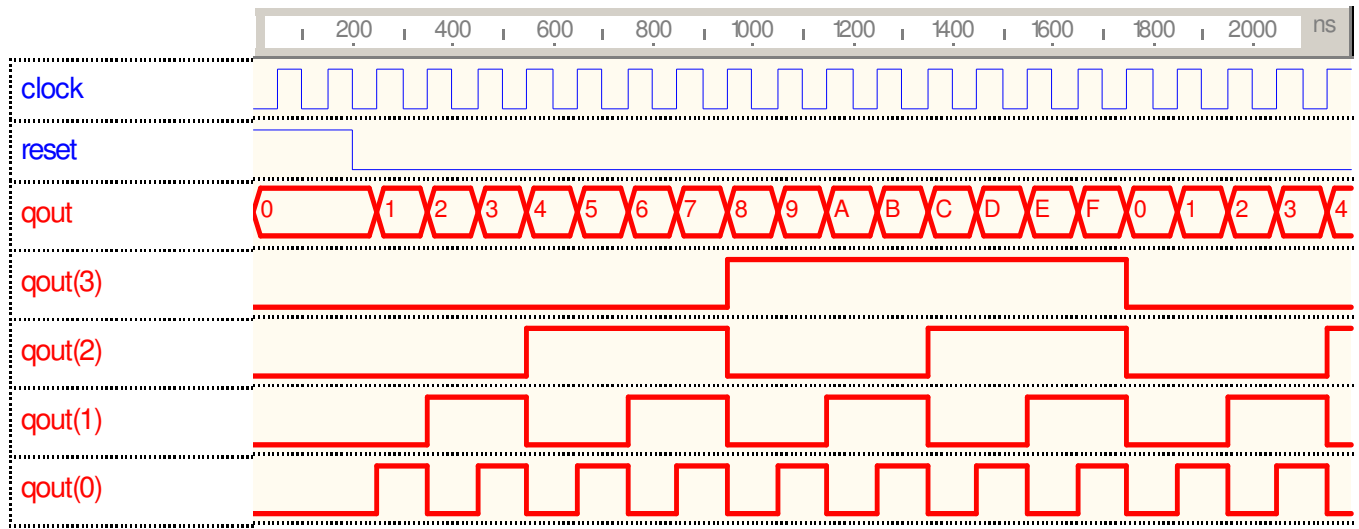

Waveforms for 4-Bit BCD Up Counter

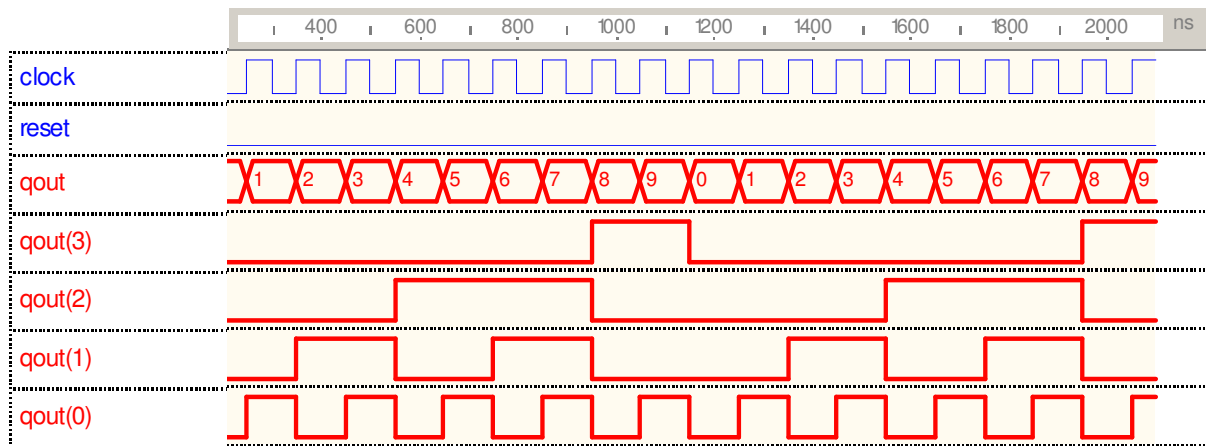

Waveforms for 4-Bit Gray Counter

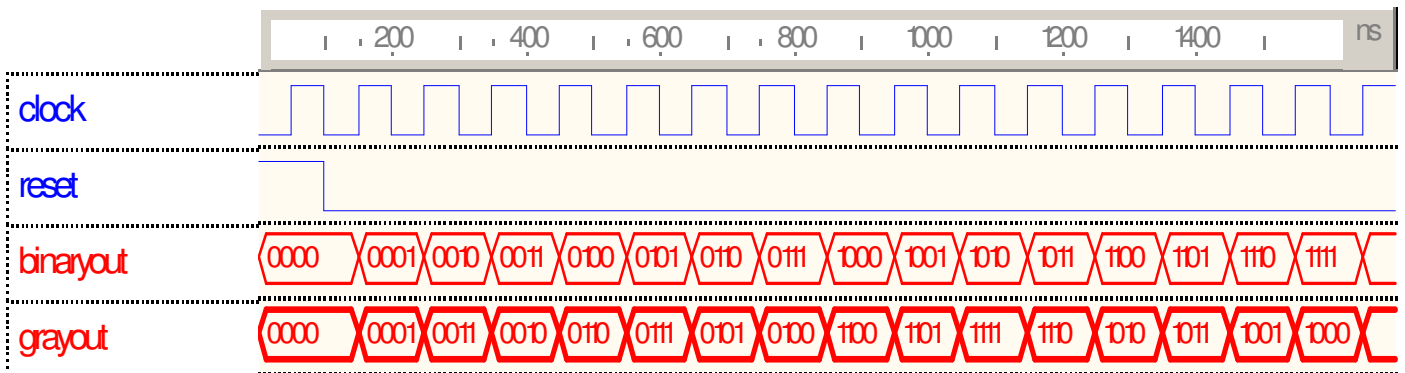

Experiment 7: Write VHDL code to display messages on the given seven-segment display interface.

7-Segment display can display the digits 0-9 and the hex extension (A-F). A signal-character displays bring out leads for 7-segments & the common elect code (Common cathode & common anode).Here in FPGA/CPLD board to interface one 7-segment LED display whose elements are connected to any I/O pins of the FPGA/CPLD.


Here we can consider common-anode 7-segment LED displays. The user can then ON by driving associated signal low.

Binary	a	b	c	d	e	f	g
0000	0	0	0	0	0	0	1
0001	1	0	0	1	1	1	1

VHDL LAB MANUAL


0010	0	0	1	0	0	1	0
0011	0	0	0	0	1	1	0
0100	1	0	0	1	1	0	0
0101	0	1	0	0	1	0	0
0110	0	1	0	0	0	0	0
0111	0	0	0	1	1	0	1
1000	0	0	0	0	0	0	0
1001	0	0	0	0	1	0	0
1010	0	0	0	1	0	0	0
1011	1	1	0	0	0	0	0
1100	0	1	1	0	0	0	1
1101	1	0	0	0	0	1	0
1110	0	1	1	0	0	0	0
1111	0	1	1	1	0	0	0

Interfacing Diagram:

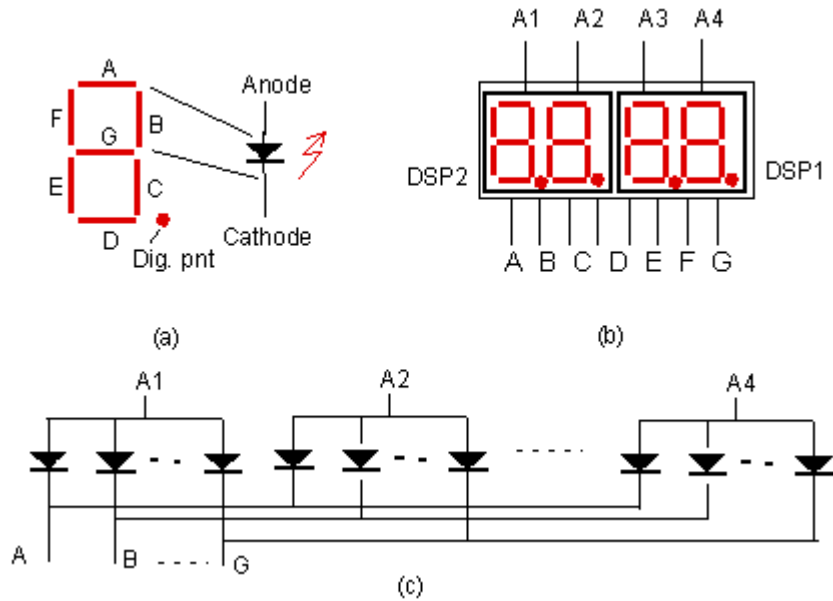

- (a) LED segments
- (b) Four displays with common anode and
- (c) LED connection on CPLD or FPGA Board.

Turning on an LED:

 

$$R = \frac{\text{voltage}}{\text{current}} = \frac{5 - 1.7}{15 \times 10^{-3}} = 220 \text{ ohms}$$

(For +5V)

Note: If your Seven-segment LED is having Digit point, Then turn on with giving Logic '1' to dig.pt permanently when particular Seven-segment is enabled.

VHDL Code for 7-Segment Displays:

```
-----  
-- File           :      seg7dec.vhd  
-- Entity         :      seg7dec  
-----  
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C  
-- Simulators     :      Mentor Graphics Modelsim OR Active HDL  
-- Synthesizers   :      Xilinx ISE  
-- Target Device  :      Spartan II or XC Series  
-----  
-- Description    :      7-Segment Decoder  
-----  
--The IEEE standard 1164 package, declares std_logic, etc.  
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.std_logic_arith.all;  
use IEEE.std_logic_unsigned.all;  
----- Entity Declarations -----  
  
entity seg7dec is  
    port (Q       : in STD_LOGIC_VECTOR(3 downto 0);  
          AtoG    : out STD_LOGIC_VECTOR(6 downto 0)  
          );  
end seg7dec;  
architecture seg7dec_arch of seg7dec is  
begin  
    process(Q)  
    begin  
        case Q is  
            when "0000" => AtoG <= "0000001";  
            when "0001" => AtoG <= "1001111";  
            when "0010" => AtoG <= "0010010";  
            when "0011" => AtoG <= "0000110";  
            when "0100" => AtoG <= "1001100";  
            when "0101" => AtoG <= "0100100";
```

```


when "0110" => AtoG <= "0100000";
when "0111" => AtoG <= "0001101";
when "1000" => AtoG <= "0000000";
when "1001" => AtoG <= "0000100";
when "1010" => AtoG <= "0001000";
when "1011" => AtoG <= "1100000";
when "1100" => AtoG <= "0110001";
when "1101" => AtoG <= "1000010";
when "1110" => AtoG <= "0110000";
when others => AtoG <= "0111000";

end case;
end process;

end seg7dec_arch;

```

Simulator waveforms for 7-Segment Displays:

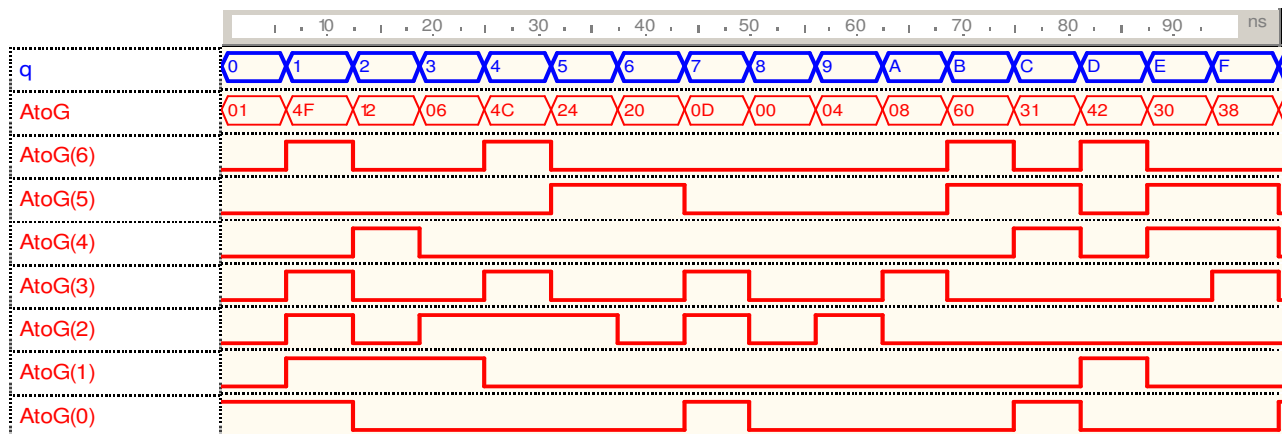

Experiment 8: Write a VHDL codes to display messages on given LCD panel.

The LCD should be initialize before displaying any characters, the initialization procedures for my LCD driver are:

1. Function set - set 8 bit long data interface
2. Display on - set display on, cursor on, and blink on.
3. Entry mode set - set entry mode to increment the cursor after a character is displayed.
4. Display Clear - clear the LCD display.

Important things about LCD timings are:


1. The LCD should have at least 1.64ms to process clear or home instruction and 40us to

VHDL LAB MANUAL

process any other instructions.

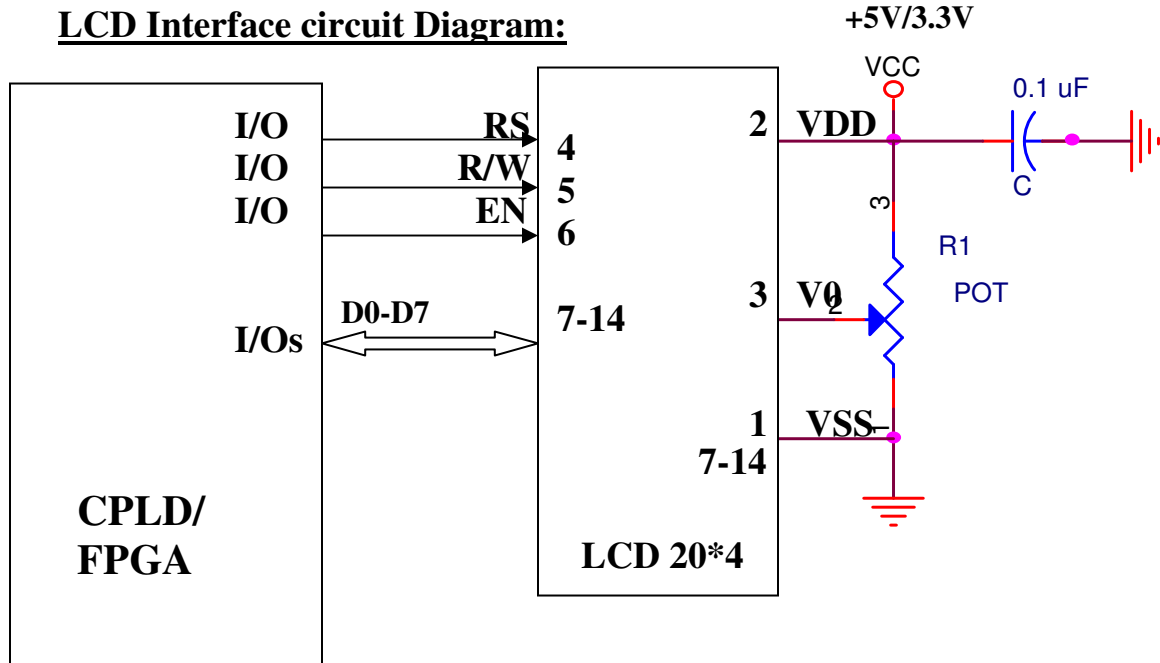2. When the register select signal is changed, there should be a 140ns address setup time before the enable signal is set to 1.
3. When displaying char. on the LCD, enable signal should have be 1 for at least 450ns.
4. The data setup time and data hold time should be at least 195ns and 10ns respectively.

The ASCII representations of each individual character are being entered into the program and displayed on to the LCD screen



Pin out of LCD and Description of each pins:

Pin No.	Signal Name	Input/Output	Function
1	VSS	Input	Ground
2	VDD	Input	+5V
3	VEE	Input	Contrast Adjust
4	RS	Input	Signal to select registers '0' : instruction register (for write) Busy flag : address counter (for read)

VHDL LAB MANUAL

			'1' : Data register (for read and write)
5	R/W	Input	Signal to select read (R) and write (W) '0' : Write '1' : Read
6	Enable	Input	Operation start signal for data read/write
7-14	DB0-DB7	Input/Output	8 bit bidirectional three-state data bus lines. Used for data transfer between FPGA and LCD

Instructions for Initialization of LCD:

Instruction	RS	R/W	DB7	DB6	DB5	DB4	DB3	DB2	DB1	DB0	Description	Execution Time (Max)
Clear Display	0	0	0	0	0	0	0	0	0	1	Clear entire display and sets DD RAM address 0 in address counter.	1.64 ms
Return Home	0	0	0	0	0	0	0	0	1	X	Sets DD RAM address 0 in address counter. Also returns display being shifted to original position. DD RAM contents remain unchanged.	1.64 ms
Entry Mode Set	0	0	0	0	0	0	0	1	I/D	S	Sets cursor move direction and specifies shift of display. These operations are performed during data write and read.	40 us
Display On/Off Control	0	0	0	0	0	0	1	D	C	B	Sets ON/OFF of entire display (D), cursor ON/OFF (C), and blink of cursor position character (B).	40 us
Cursor or Display Shift	0	0	0	0	0	1	S/C	R/L	X	X	Moves cursor and shifts display without changing DD RAM contents	40 us
Function Set	0	0	0	0	1	DL	N	F	X	X	Sets interface data length (DL), number of display lines (L)	40 us

VHDL LAB MANUAL

											and character font (F).	
Set CG RAM Address	0	0	0	1	ACG						Sets CG RAM address. CG RAM data is sent and received after this setting.	40 us
Set DD RAM Address	0	0	1	ADD						Sets DD RAM address. DD RAM data is sent and received after this setting	40 us	
Read Busy Flag & Address	0	1	BF	AC						Reads Busy flag (BF) indicating internal operation is being performed and reads address counter contents.	0 us	
Write Data to CG or DD RAM	1	0	Write Data						Writes data into DD RAM or CG RAM	40 us		
Read Data from CG or DD RAM	1	1	Read Data						Reads data from DD RAM or CG RAM	40 us		
	I/D = 1 : Increment I/D = 0 : Decrement S = 1 : Accompanies display shift S/C = 1 : Display shift S/C = 0 : Cursor move R/L = 1 : Shift to the right R/L = 0 : Shift to the left DL = 1 : 8 bits, DL = 0 : 4 bits N = 1 : 2 lines, N = 0 : 1 lines F = 1 : 5*10 dots, F = 0 : 5*7 dots BF = 1 : Internally operating BF = 0 : Can accept instruction X : Don't Care									DD RAM : Display data RAM CG RAM : Character generator RAM ACG : CG RAM address ADD : DD RAM address : Corresponds to cursor address AC : Address counter used for both DD and CG RAM address		

Notes:

- After power on, the LCD has to wait more than 15 ms for Vcc rises to 4.5V before accepting the first instruction.

VHDL LAB MANUAL

- I set signal "count" count from 0 to 3. However, this value is depend on the system clock. Make sure the LCD has enough time to execute the next instruction. Execution time for each instruction(Follow the instruction table).

- **VHDL example for LCD display Initialization**

```
-----  
-- File                :    lcd_init.vhd  
-- Entity              :    lcd_init  
-----  
-- University         : Directorate of Technical Education, VLSI Design Lab V E&C  
-- Simulators         :    Mentor Graphics Modelsim OR Active HDL  
-- Synthesizers       :    Xilinx ISE  
-- Target Device      :    Spartan II or XC Series  
-----  
-- Description        :    This program initialize the LCD display  
-----  
--The IEEE standard 1164 package, declares std_logic, etc.  
library IEEE;  
use IEEE.Std_Logic_1164.all;  
use IEEE.Std_Logic_unsigned.all;  
use IEEE.NUMERIC_STD.all;  
----- Entity Declarations -----  
entity lcd_init is  
  
    generic(width : positive := 8);  
    port(reset, clock, enable, done_ack : in std_logic;  
         done, RW, rs, lcd_e : out std_logic;  
         Qout : buffer std_logic_vector(width-1 downto 0)  
         );  
  
end lcd_init;  
  
architecture initial of lcd_init is  
  
    type state_type is (waiting, i0, i1, i2, i3, donestate);  
    signal state, next_state : state_type;  
    signal count,count_temp : std_logic_vector(1 downto 0);  
    signal Qout_temp : std_logic_vector(width-1 downto 0);  
  
begin  
  
    running : process(state,enable,done_ack,count) is  
  
        begin
```

VHDL LAB MANUAL

case state is

```
when waiting =>
done <= '0';
lcd_e <= '1';
RW <= '0';
rs <= '0';
Qout_temp <= "00000000";

if enable = '1' then
    next_state <= i0;
else
    next_state <= waiting;
end if;

when i0 =>
Qout_temp <= "00000001"; --clear display

if count = "11" then
    next_state <= i1;
else
    next_state <= i0;
end if;

when i1 =>
Qout_temp <= "00000010"; --clear display & returns to HOME
if count = "11" then
    next_state <= i2;
else
    next_state <= i1;
end if;

when i2 =>
Qout_temp <= "00111000"; --2 line display

if count = "11" then
    next_state <= i3;
else
    next_state <= i2;
end if;

when i3 =>
Qout_temp <= "00001110"; --truns on display with cursor at home

if count = "11" then
    next_state <= donestate;
```

VHDL LAB MANUAL

```
else
    next_state <= i3;
end if;

when donestate =>
done <= '1';
Qout_temp <= ( others => '0' );

if done_ack = '1' then
    next_state <= waiting;
else
    next_state <= donestate;
end if;

end case;

end process running;

timing : process(clock,reset) is

begin


    if rising_edge(clock) then
        Qout <= Qout_temp;
        count <= count_temp;
        if reset = '1' then
            state <= waiting;
            count_temp <= "00";
        else
            state <= next_state;
            count_temp <= count_temp + "01";
        end if;
    end if;

end process timing;

end initial;
```

- **Simulator waveforms for LCD display Initialization:**


VHDL LAB MANUAL

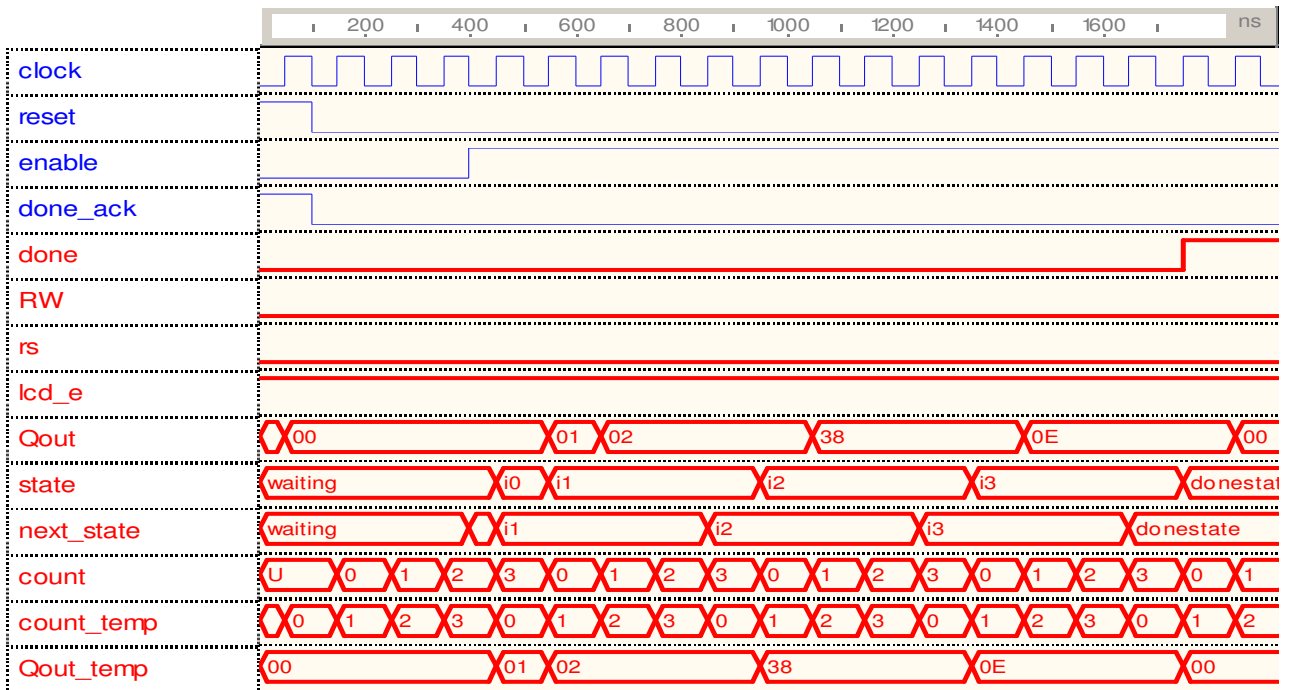

Experiment 9: Write codes to operate the given stepper motor.

Stepper motors are electromechanical devices Which converts a digital pulses in mechanical rotation, that provide accurate incremental rotation.

The most common stepper motor uses four windings for a four-phase operation. A typical four-phase motor driving circuit is shown in Figure using an FPGA to generate the sequence logic. The clock (CLK) input synchronizes the logic and determines the speed of rotation. The motor advances one step per clock period; the angle of rotation of the shaft will depend on the particular motor. To determine the clock period, consider that the stepper motor torque increases as frequency decreases. The direction (DIR) control input changes the sequence at the outputs (PH1 to PH4) to reverse the motor direction. The enable input (EN) determines whether the motor is rotating or holding. The active low reset input (RST) initializes the circuit to ensure that the correct starting sequence is provided to the outputs.. The enhanced sequence provides increased torque but requires twice the current.

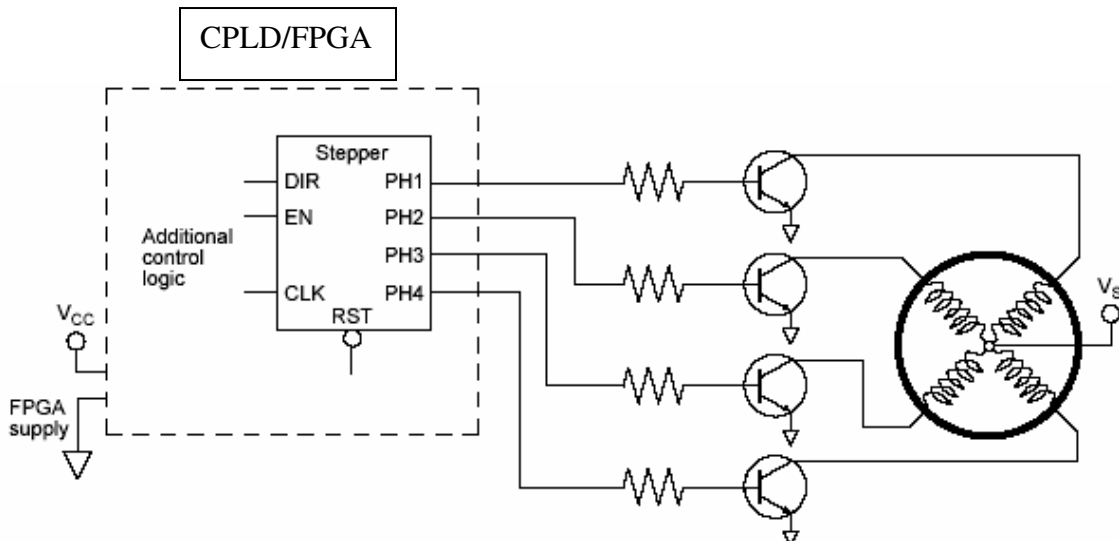

Note: Please go through the datasheet or Voltage and Current ratings of stepper motor and

Decide The transistor selection depends on drive current, power dissipation, and gain.(Preferably NPN Power Darlington transistors).

The series resistors should be selected to limit the FPGA current to 8 mA per output, 1/4 Watt resistors Value.

Typical Ratings available stepper motor are:

1. The four windings have a common connection to the motor supply voltage (**VS**), typically ranges **from 5 to 30 Volts**.
2. Each motor phase current may range from **100 mA to as much as 10 A**.

Stepper motor sequencing: There are several kinds of sequences that can be used to drive stepper motors. The following tables give the most common sequences for energizing the coils. Following the steps in ascending order drives the motor in one direction, going in descending order drives the motor the other way. This sequence interleaves the normal and wave sequences.

If step angle = 1.8, For One revolution $360/1.8=200$ steps(In Full step mode)

If step angle = 0.9, For One revolution $360/0.9=400$ steps(In Half step mode)
Bipolar stepper motor will not run in Half step mode for any consult the stepper motor manufacturer.

Full step

Steps	Q1	Q2	Q3	Q4
Step0	1	0	1	0
Step1	1	0	0	1
Step2	1	0	1	0
Step3	0	1	1	0

Make this sequence in Descending order motor rotates in opposite direction(This sequence will be provided by the stepper motor manufacturer).

VHDL Code Uni-polar Stepper Motor Controller in Full step mode:

```

-----
-- File           : SMControl.vhd
-- Entity         : SMControl
-----
-- University     : Directorate of Technical Education, VLSI Design Lab V E&C
-- Simulators     : Mentor Graphics Modelsim OR Active HDL
-- Synthesizers   : Xilinx ISE
-- Target Device  : Spartan II or XC Series
-----
-- Description    : Uni-polar Stepper Motor Controller in Full step ---
--               : mode
-----
--The IEEE standard 1164 package, declares std_logic, etc.
library IEEE;
use IEEE.Std_Logic_1164.all;
use IEEE.NUMERIC_STD.all;
----- Entity Declarations -----
-- NOTE : Ask the stepping sequence from stepper motor manufacturer
--        and change your VHDL code this sequence commonly used
-----

entity SMControl is
    Port (Clk,Reset,E,Dir: in std_logic;
          Sec : out std_logic_vector(3 downto 0)
    );
end SMControl;
architecture Behavioral of SMControl is
    Type States is (Step_0, Step_1, Step_2, Step_3);
    Signal Next_State, Current_State : States;
begin
    Process( Clk, Reset, Current_State )
    Begin
        if Reset = '1' then
            Next_State <= Step_0;
        elsif Clk'event and Clk = '1' then
            Case Current_State is
                When Step_0 =>
                    Sec <= x"A";
                    if E = '1' then
                        Next_State <= Step_0;
                    else
                        If DIR = '1' then

```

VHDL LAB MANUAL

```


        Next_State <= Step_1;
    Else
        Next_State <= Step_3;
    End if;
end if;
When Step_1 =>
    Sec <= x"9";
    if E = '1' then
        Next_State <= Step_1;
    else
        If DIR = '1' then
            Next_State <= Step_2;
        Else
            Next_State <= Step_0;
        End if;
    end if;
When Step_2 =>
    Sec <= x"5";
    if E = '1' then
        Next_State <= Step_2;
    else
        If DIR = '1' then
            Next_State <= Step_3;
        Else
            Next_State <= Step_1;
        End if;
    end if;
When Step_3 =>
    Sec <= x"6";
    if E = '1' then
        Next_State <= Step_3;
    else
        If DIR = '1' then
            Next_State <= Step_0;
        Else
            Next_State <= Step_2;
        End if;
    end if;
When Others =>
    Next_State <= Step_0;
end Case;
end if;
end Process;
Process(Clk)
Begin
    if Clk'event and clk = '1' then
        Current_State <= Next_State;
    end if;
end if;
```

```


end process;
end Behavioral;

```

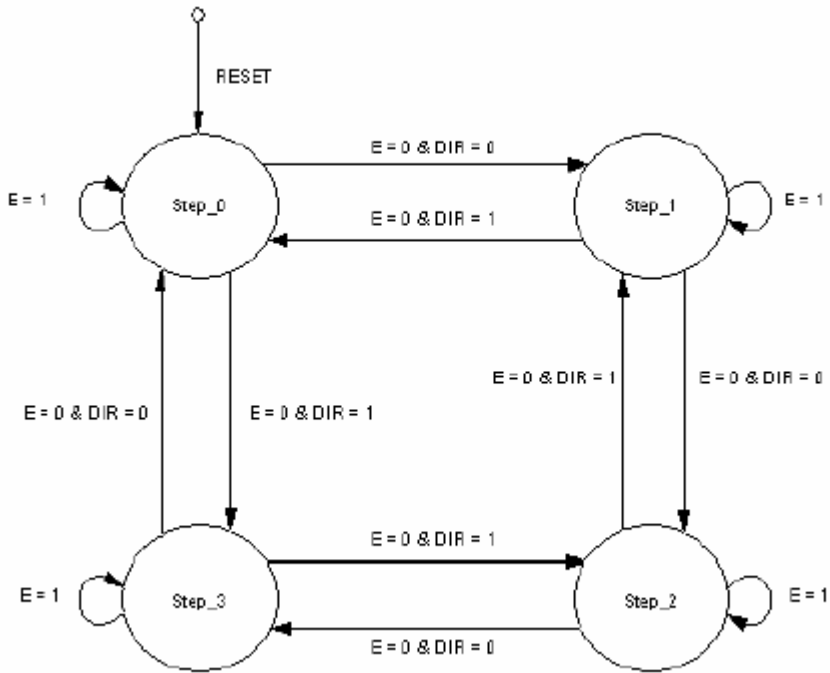State machine Diagram according to step changes:



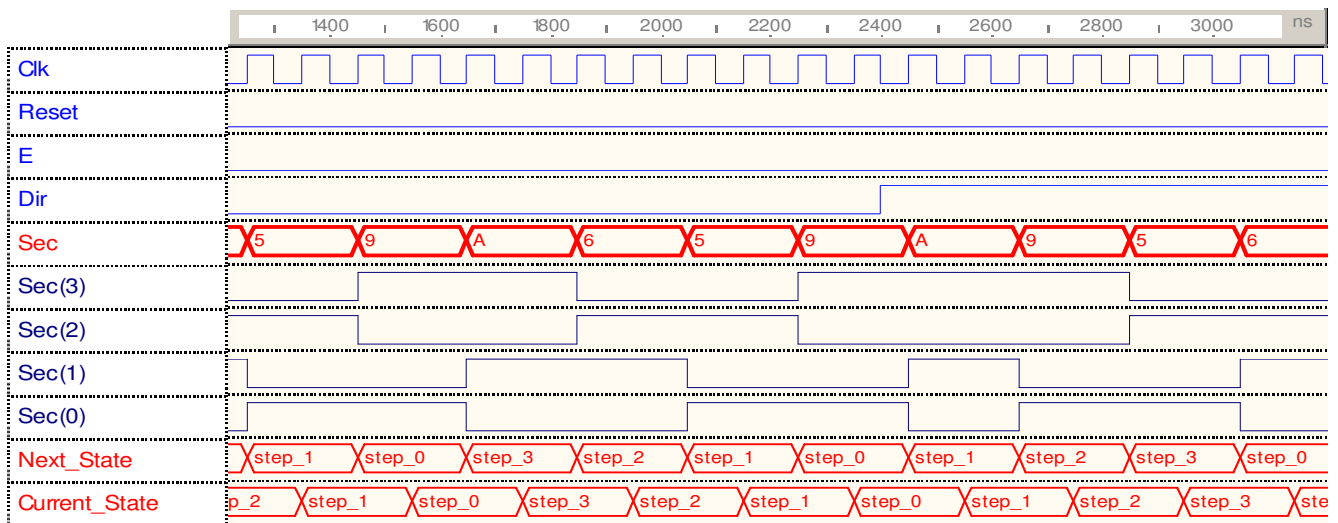Simulator waveforms for Uni-polar Stepper Motor Controller in Full step mode:



VHDL LAB MANUAL